

Keywords: boost, controller, step-up, step up, DC-DC, PFM, efficiency

APPLICATION NOTE 1054

Simple Change Improves PFM Boost-Controller Efficiency

Apr 15, 2002

Abstract: Modification to the standard PFM boost-controller circuit provides a 5% efficiency improvement at medium and light loads.

A simple modification to the standard application circuit for a high-efficiency PFM boost controller (**Figure 1**) yields even higher efficiency. By increasing the value of R_{SENSE} and connecting the output filter capacitor to the current-sense pin (CS) instead of ground, the circuit's current limit is made dependent on load current. The result is lower I^2R loss (in the inductor, MOSFET, and output-capacitor ESR), which gives better efficiency for light-to-medium loads.

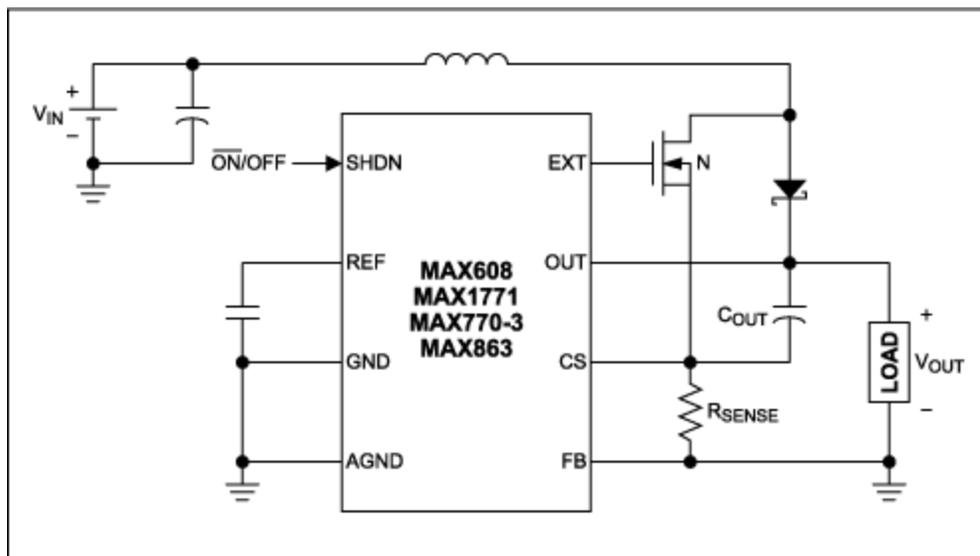


Figure 1. Connecting the C_{OUT} capacitor to CS instead of ground causes load-dependent current limiting, which reduces I^2R loss.

Connecting the filter capacitor to CS allows R_{SENSE} to monitor the inductor current constantly—via the MOSFET during t_{ON} and via the diode and filter capacitor during t_{OFF} . During t_{ON} , the filter-capacitor voltage drives load current in a loop ($C_{OUT}/LOAD/R_{SENSE}$) that opposes the inductor current through R_{SENSE} . In effect, the CS node subtracts load current from inductor current during this interval. Thus, as load current increases, the higher level of inductor current required to produce 100mV across R_{SENSE} extends the t_{ON} interval and raises the current limit:

$$I_{LIM} = (100\text{mV}/R_{SENSE}) + I_{LOAD}$$

This modification does not affect the quiescent current and requires no additional circuitry, but the voltage waveform at CS couples through C_{OUT} to the output, increasing the output ripple about 100mV for light to medium loads. To obtain a lower peak current and higher efficiency for light to medium loads, the value of R_{SENSE} should be increased as necessary to obtain the same current limit at maximum load as that provided by the standard application circuit. **Figure 2** shows the effect of a load transient on the inductor current and output ripple, and **Figure 3** shows efficiency gains over the standard connection.

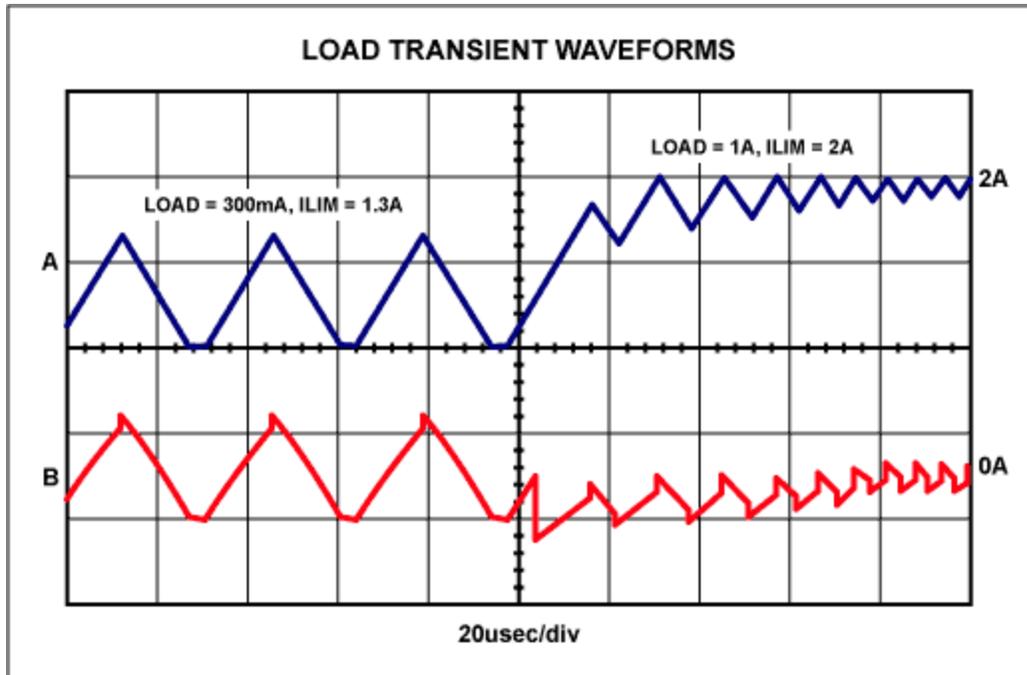


Figure 2. An abrupt change in load current (300mA to 1A) causes changes as shown in the inductor current (top trace, 1A/div) and V_{OUT} ripple (ac-coupled bottom trace, 100mV/div).

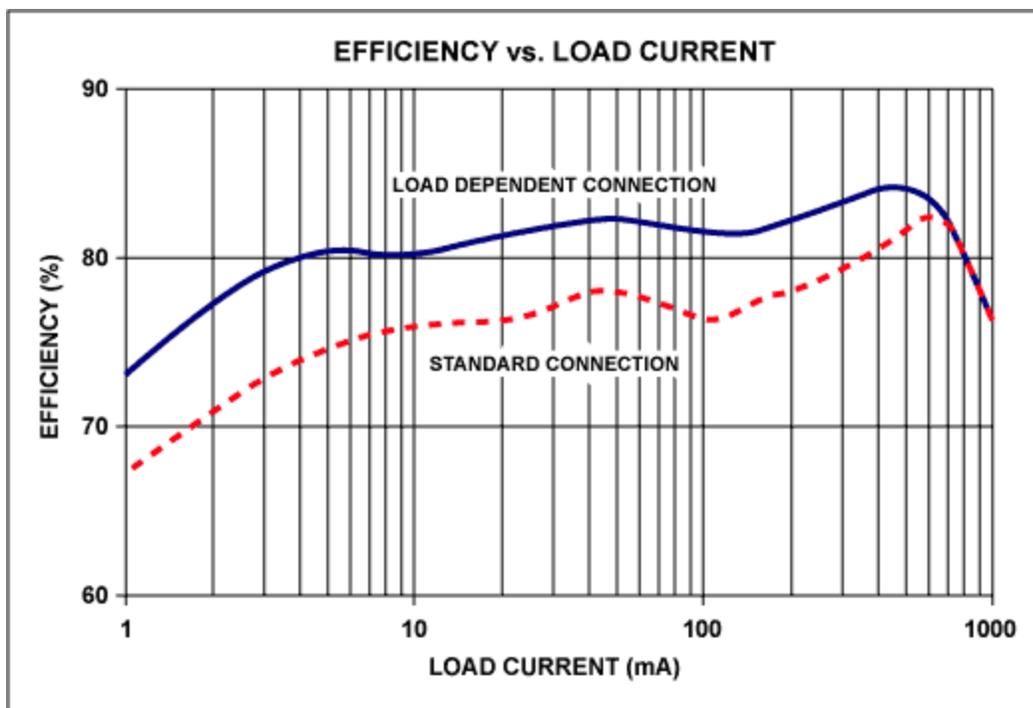


Figure 3. Efficiency for the Figure 1 circuit is 4-5% better than that of a standard connection.

Related Parts

MAX1771	12V or Adjustable, High-Efficiency, Low I_Q , Step-Up DC-DC Controller	Free Samples
MAX608	5V or Adjustable, Low-Voltage, Step-Up DC-DC Controller	Free Samples
MAX863	Dual, High-Efficiency, PFM, Step-Up DC-DC Controller	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1054: <http://www.maximintegrated.com/an1054>

APPLICATION NOTE 1054, AN1054, AN 1054, APP1054, Appnote1054, Appnote 1054

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>