



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Interface Circuits](#) > APP 1076

Keywords: RS-485, rs484, EIA/TIA-485, fail-safe, variable-reluctance sensor, low-speed, medium speed, ESD protected, rs485 transceiver

APPLICATION NOTE 1076

Fail-Safe, Low-Speed, Variable-Reluctance Sensors

By: **Phill Leyva**
May 24, 2002

Abstract: Technical brief describes construction of a variable-reluctance sensor for detecting low- or medium-speed events. A simple circuit is shown utilizing two channels of an ESD-protected RS-485 transceiver to deliver differential output data capable of providing fail-safe signals indicating sensor or cable malfunction.

Variable-reluctance (VR) sensors are preferred for industrial and automotive environments because they withstand mechanical vibration and high-temperature operation up to 300°C. In most applications, they sense a steel target that is part of a rotating assembly. Because the unprocessed signal amplitude is proportional to target speed, a sensor whose signal-processing circuitry is designed for high speed will cease to function as rotation slows.

Hall-effect sensors are preferred for lower speeds (several pulses per second), but they require that a magnet be attached to the rotating assembly, making them prone to failure when the magnet is broken or damaged. Neither type (VR or Hall-effect) offers fail-safe detection of the processed signal in the event of failure in the cable or sensor.

The circuit of **Figure 1** is a fail-safe VR sensor suitable for low- to medium-speed operation. Comprising of L1, R1, and a quad RS-422/RS-485 receiver (IC1), it provides the complementary, independent output signals VOUT and Active-Low VOUT. Table 1 lists the resulting fail-safe modes. Supply voltage can be +10V, +12V, or the control system's +24V DC source.

Y1 and Y2 can source up to 10mA of current. They alternately switch the logic-rated n-channel MOSFETs Q1 and Q2, which in turn provide VOUT and Active-Low VOUT. An LDO voltage regulator (IC2) generates the +5VDC required by IC1. **Figure 2** illustrates low- and medium-speed operation for the sensor.

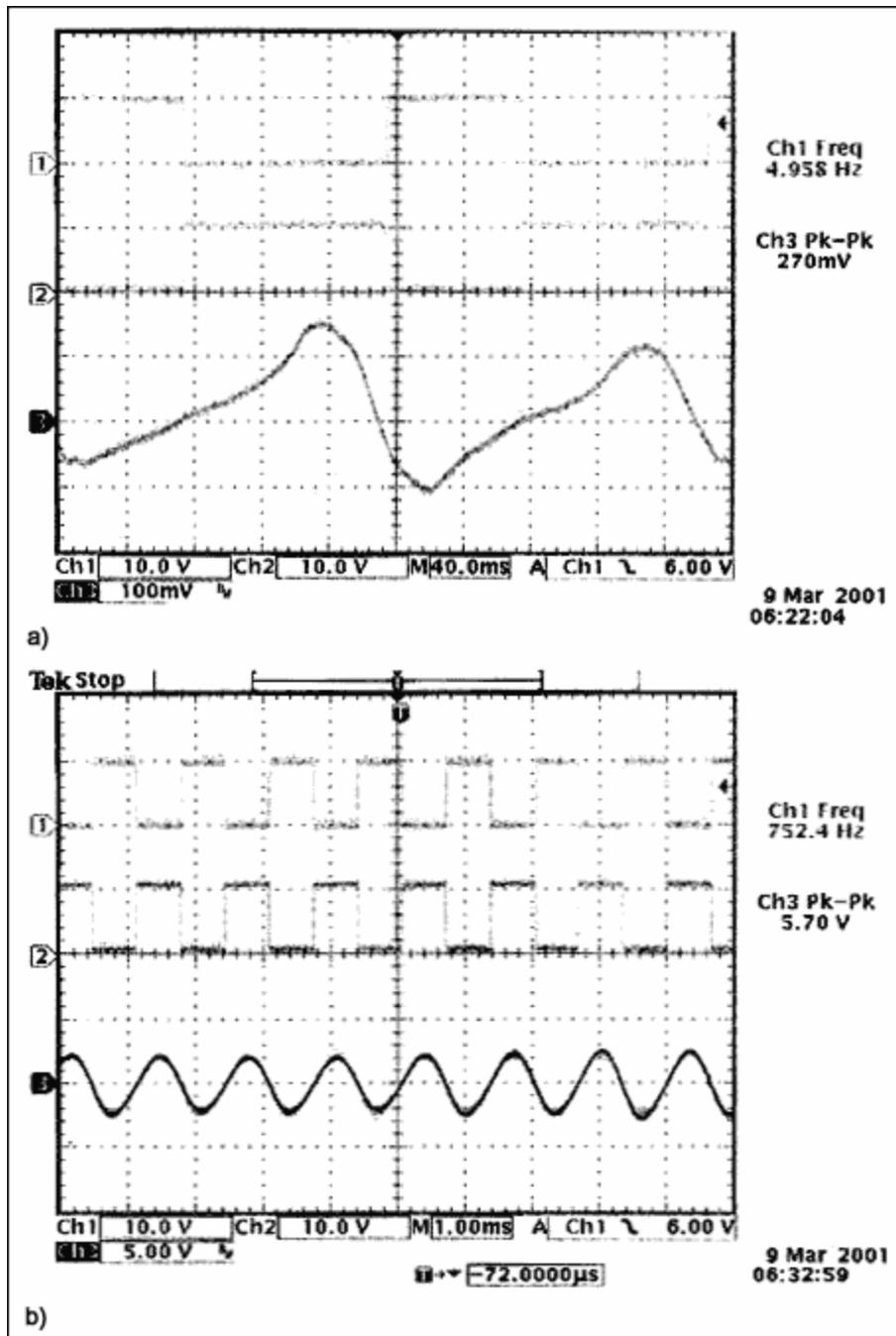


Figure 2. These Figure 1 waveforms, produced by two targets 180° apart, illustrate low- and medium-speed operation: 4.9Hz at 2.4 revolutions/sec (a), and 752.4Hz at 376.2 revolutions/sec (b). Channel 1 is VOUT, Channel 2 is Active-Low VOUT, and Channel 3 is the voltage across R1.

For +5V-supply applications in which a microcontroller can be located close to the sensor, only L1, R1,

and IC1 are required for a direct interface. For +3V applications, replace IC1 with a MAX3096 IC.

A similar version of this article appeared in the November 22, 2001 issue of *EDN* magazine.

Related Parts

MAX3095	±15kV ESD-Protected, 10Mbps, 3V/5V, Quad RS-422/RS-485 Receivers	Free Samples
MAX3096	±15kV ESD-Protected, 10Mbps, 3V/5V, Quad RS-422/RS-485 Receivers	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1076: <http://www.maximintegrated.com/an1076>

APPLICATION NOTE 1076, AN1076, AN 1076, APP1076, Appnote1076, Appnote 1076

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>