

Keywords: Programmable Universal Filter Implements C-Message Weighting Function

## APPLICATION NOTE 11

# Programmable Universal Filter Implements C-Message Weighting Function

Jul 09, 1998

The C-message filter, which simulates the frequency response of the human ear, is a commonly specified test and measurement filter for voice, audio, and telecommunication applications in the U.S. In Europe, a close relative is a psophometric noise-weighting filter. You can construct either type by cascading three 2nd-order bandpass sections with a 2nd-order lowpass section. The C-message filter, for example, is shown in **Figure 1**

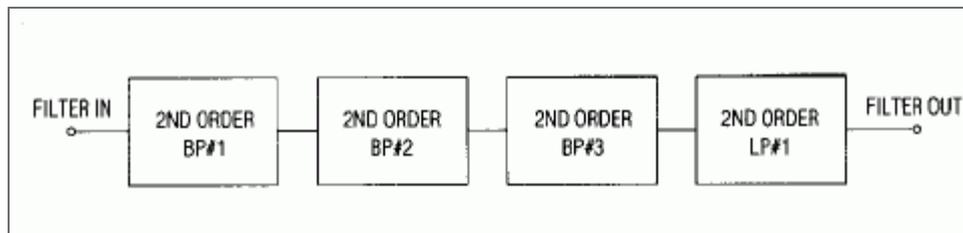


Figure 1. Cascaded, 2nd-order universal filter sections implement a C-message filter.


Dual universal, 2nd-order IC filters provide a compact and efficient means for implementing the circuit of Figure 1. If the IC filters are programmable, switched-capacitor types as shown, you can rapidly implement a C-message, psophometric, or other test filteres on demand simply by loading the chips with different sets of coefficients. These coefficients set each 2nd-order section's filter mode, Q, and cutoff or center frequency  $f_0$ . The C-message filter has poles only, which are specified by the IEEE Standard 743-1984:

Table 1.

Pole	Value in rad/sec	Value in Hz ( $f_0$ )	Q
BP#1	-1502 j1267	312.741	0.6540
BP#2	-2439 j5336	933.761	1.2027
BP#3	-4690 j15267	2541.886	1.7026
LP#1	-4017 j21575	3492.778	2.7316

**Figure 2** shows the external connections that configure two filter ICs in the architecture of Figure 1, along with a table of decimal equivalents for the digital coefficients associated with each filter section. These 2nd-order sections establish pole locations in accordance with the  $f_0$  values listed. Each section contains two continuous-time Chebyshev filters whose center frequency can be digitally programmed in 128 steps over the range 1 to 25kHz. Passband ripple is 0.1dB. For maximum signal-to-noise ratio, the signal amplitude at

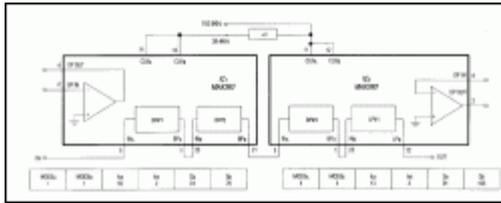each section output should be as high as possible.




[More Detailed Image](#)

Figure 2. The circuit connections and coefficient sets shown enable two programmable, switched-capacitor filter ICs to realize the C-message filter of Figure 1. By loading the ICs with different coefficient sets, you can obtain the European psophometric noise-weighting filter and other test/measurement filters.

Signal swings are as follows: If you apply 4V to input  $IN_A$  on IC<sub>1</sub>, output  $BP_A$  swings 2.7V, output  $BP_B$  swings 1.85V, output  $BP_A$  of IC<sub>2</sub> swings 1.6V, and the lowpass output ( $LP_A$  of IC<sub>2</sub>) swings 3.2V. IC<sub>2</sub> operates in mode 4 instead of mode 1, which provides a gain of 2 instead of 1 for the LP and BP outputs (see data sheet)

You must bandlimit the filter's input signal to  $f_{CLK}/4$  or less, where (in this case)  $f_{CLK} = 38.4kHz$ . The uncommitted op amp in IC<sub>1</sub> can provide second- or 3rd-order lowpass filter for this purpose. The uncommitted op amp in IC<sub>2</sub> can provide a similar lowpass filter for smoothing the output signal.

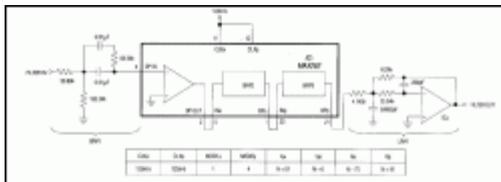As an alternative, you can realize the C-message function using one filter IC and an external op amp (Figure 3). This approach lacks flexibility, however. You can no longer switch to other filter functions by electrically reprogramming the circuit.



[More Detailed Image](#)

Figure 3. This circuit, based on one filter IC and an external op amp, produces the same C-message response of Figure 1 but lacks programming flexibility.

This circuit realizes the first bandpass (BP#1) in terms of external resistors and capacitors around uncommitted opamp of IC<sub>1</sub>. BP#1, which also serves as an antialiasing filter for the sampling action of IC<sub>1</sub>, is an infinite-gain, multiple-feedback bandpass filter with  $f_0 = 312.74Hz$ ,  $Q = 0.654$ , and gain = 0.654. Design procedures for this configuration are available in the literature.

IC<sub>2</sub> implements BP#2 and BP#3 with the same gain and signal levels as in Figure 1. The external op amp with resistors and capacitors implements LP#1, which also serves as the output smoothing filter. Like BP#1 you can design LP#1 as an infinite-gain, multiple-feedback circuit with  $f_0 = 3492.778Hz$ ,  $Q = 2.7316$ , and gain = 2.

The 125kHz clock frequency is arbitrary; other values require that you program IC<sub>1</sub> for a different  $f_{CLK}/f_0$  ratio.

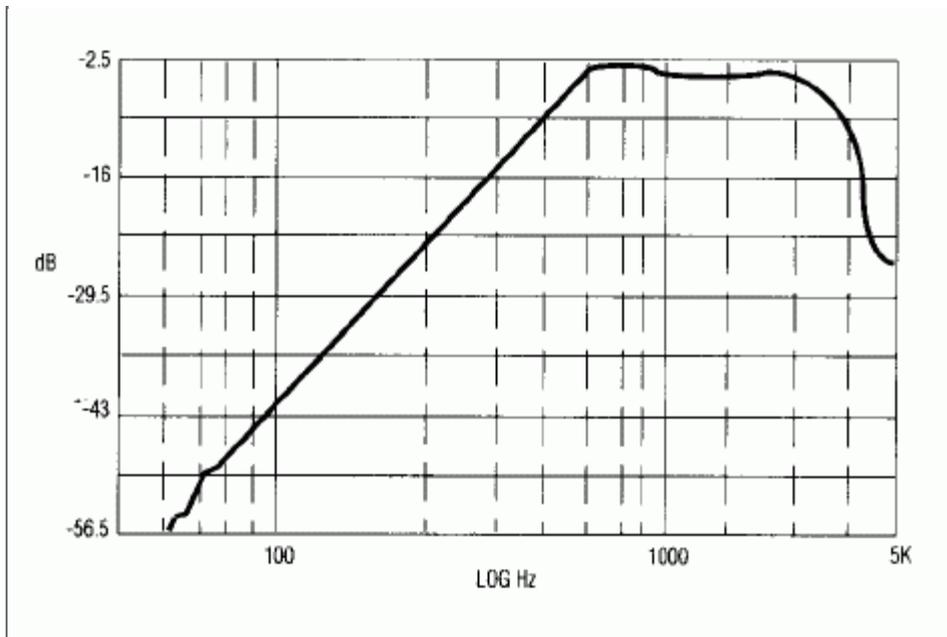


Figure 4. Circuits in Figure 1 and Figure 2 produce the same frequency response.

In both filter circuits (Figure 1 and Figure 2) the coefficients for  $f_{0A}$ ,  $f_{0B}$ ,  $Q_A$ ,  $Q_B$  were calculated by software available from Maxim (see data sheet). **Figure 4** shows the filter transfer function for either realization.

#### Related Parts

[MAX262](#)

Microprocessor Programmable Universal Active Filters

[Free Samples](#)

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 11: <http://www.maximintegrated.com/an11>

APPLICATION NOTE 11, AN11, AN 11, APP11, Appnote11, Appnote 11

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>