



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Interface Circuits](#) > APP 1846

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Protection and Isolation](#) > APP 1846

Keywords: RS232, RS 232, RS-232, low power RS 232, low voltage, EIA/TIA-562, transmitter, transceiver serial interface, 3 to 5.5V system power source, resistor isolated transceiver, isolated data interface, external filter, power-transfer capacitors

#### APPLICATION NOTE 1846

# Using the MAX3250 $\pm 50V$ -Isolated RS-232 Transceivers

Dec 30, 2002

*Abstract: This paper describes how resistor-isolated transceivers are able to handle  $\pm 50V$  ground-offset signals, and indicates how and why the offset voltage is limited by the design. The method of transferring power across the isolation barrier is explained.*

The MAX3250 high-offset-voltage (high- $V_{OS}$ ) rejection RS-232 transceiver provides a  $\pm 50V$  isolated data interface and power for the line-side transceiver circuits. Unlike optically- or transformer-isolated RS-232 transceivers, its main features are low cost, an allowed  $\pm 50V$  resistive-isolation character in a single small IC package, and capacitive power transfer from non-isolated to isolated-side circuitry. It operates from a single +3.3 or +5V system-power source, and requires only external surface-mount capacitors for operation. An overall low profile is maintained when compared to other isolation techniques requiring opto-couplers and/or a transformer.

This paper describes how resistor-isolated transceivers are able to handle  $\pm 50V$  ground-offset signals, and indicates how and why the offset voltage is limited by the design. The method of transferring power across the isolation barrier is explained.

## Pseudo-Isolated RS-232 Transceiver

The MAX3250 provides a  $\pm 50V$  isolated data interface while, in the same IC package, providing isolated power for the line-side transceiver circuits from a single +3 to +5.5V system power source. The detailed functional diagram in **Figure 1** allows a clear visualization of the isolation, power-transfer, and protection circuits. External filter, charge-pump, and power-transfer capacitors are utilized.

 


Figure 1. MAX3250 functional block diagram.

When RS-232 cables connect between buildings, the originating signal common or ground may not be at the same electrical potential as that of the receiving-location ground. Typically, the drive-circuit common is connected to chassis or frame ground either directly or through a 100Ω resistor. Hence, the situation illustrated graphically in **Figure 2** may exist.

 


Figure 2. Offset voltages in two-wire line data-transmission system.

The ISO COM and the data line will take on an offset voltage equal to the vector sum of the ground-potential difference and any longitudinally-coupled noise voltage generated along the signal path between transmitter and receiver.

$$V_{OS} = e_{GD} + e_{LC}$$

Eq. 01

The receiving-location ground potential may differ substantially from the potential at the driver-location, and it is the difference between the two that is of interest when considering application of the MAX3250. This offset voltage ( $V_{OS}$ ) must be isolated from the logic side of the MAX3250.

## How High-Offset-Voltage Transceivers Work

High- $V_{OS}$  data transceivers include no truly isolated circuits. Instead, they separate logic-side circuitry from line-side circuitry with high-value resistive attenuators as detailed in **Figure 3**. These attenuators are typically constructed so that about 1% of the input signal reaches the attenuator output. Consequently, only 1% of the applied isolation voltage reaches across the resistive barrier. Separate drivers send data across the barrier in each direction where the signal is attenuated before being detected by comparators on each side of the barrier. Attenuators in the MAX3250 have a ratio of 75:1.

 


Figure 3. Resistive isolation technique.

Reference voltages are also created on each side and sent across the barrier with identical 75:1 attenuation to bias the receiving comparators which then see the same common-mode offset voltage on both signal and reference lines. As the comparators read both the attenuated signal and the attenuated reference, an offset voltage of 50V occurring on the line would only translate to a 2/3V common-mode voltage on the outputs of the resistive barriers. As long as the differential receiver can accept the 2/3V CM voltage and is sensitive enough to detect 1/75th of the differential-signal input to the resistive attenuator, the system will operate correctly.

Thus, a full bi-directional signaling system is created with 75:1 barrier attenuation of all signals to allow two-way communication and a 50V difference across the resistive barrier. This is a pseudo-isolated circuit rather than a classically isolated circuit, yet it accomplishes the isolation needed in perhaps the majority of applications.

Note that there is a resistance between ISO COM and system GND (see Figure 1) due to the existence of nine sets of isolation resistors. The approximate parallel resistance of these nine attenuators is 72k $\Omega$ .

## Power Transfer Across the Isolation Barrier

Unless a separate isolated power supply is available to operate the isolated RS-232 transceiver, power

must be transmitted from the system or non-isolated side to the line or isolated-side circuits without destroying the required isolation. It is a practical matter to use capacitive voltage transfer across the isolation barrier when the planned isolation is no more than 50-100V. Higher voltages can be isolated; but the required capacitors become somewhat large at, say, 500V. Capacitive power transfer can be accomplished by differentially driving a pair of capacitors from a square-wave oscillator on the system side as indicated in **Figure 4**. The external capacitors feed three diodes and a filter capacitor on the isolated side to produce an isolated DC output. The third diode is present to allow recharging/discharging of the coupling capacitors on alternate half-cycles of the oscillator signal. The coupling-capacitor voltage ratings are selected to be greater than the required line-side isolation or offset voltage.

 


Figure 4. Capacitor-coupled isolated supply.

The isolated-supply power-transfer system operates somewhat like the well-known charge pump. The square-wave oscillator reverses its output polarity (0 or +5V) on alternate half cycles of operation. Its output is always a square wave (50% duty cycle), but (in the MAX3250) its output resistance increases on command (via a return feedback path visible in Figure 1) when ISO V<sub>CC</sub> reaches its design voltage. Thus, it operates to provide either normal or reduced power transfer to the isolated supply. As the line-side load draws down the voltage on C6, the feed-back signal will again cause the oscillator to more effectively replenish the charge on C6. The output voltage is thus under active regulation, with some ripple on the output at a ripple frequency depending upon the actual load. A Zener diode on the output side acts as a voltage reference against which a fraction of the output is compared to drive the control signal that is sent back across the isolation barrier to the oscillator. The charge pump injects noise currents into the ISO COM terminal to create a noise voltage on ISO COM whenever ISO COM is not connected to system GND. Hence, ISO COM should be bypassed to system GND with a 10nF capacitor (C9 in Figure 4). There are two additional regulating charge pumps driven by ISO V<sub>CC</sub> to create regulated  $\pm 5.5V$  supplies for the RS-232 drivers and receivers.

## Control and Data Transfer Across the Isolation Barrier (refer to Figure 1)

Isolation is provided by the resistive isolation technique already described. Note that the shut-down (SHDN) and both transmit (T<sub>IN</sub>) signals cross the isolation barrier from left to right or from the logic side to the line side as signals referenced to a logic-side reference voltage. The two received-data (R<sub>IN</sub>) signals cross the isolation barrier from right to left or from line side to logic side as a signal referenced to a line-side reference voltage. All signals, including references, are attenuated after crossing the isolation barrier by an identical amount of 1/75 or 1.33% of signal. Each attenuated data or control signal is applied to one comparator input, and the associated attenuated reference voltage is applied to the other comparator input. The reference voltages are designed to be midway between the high and low levels of the data and control signals so that each comparator operates at maximum sensitivity.

Two more signals cross the isolation barrier from right to left. These are the previously-discussed control signal to inform the logic-side circuits that the isolated supply voltage is at its design level and a fault



 


Figure 6. Conducted noise example.

## Offset Isolation-Voltage Limits

The isolation voltage limits of the MAX3250 are determined by two characteristics.

1. The charge-pump isolation-voltage limit is set by the breakdown rating of capacitors C1, C2, and C9 (see Figure 4).
2. The data-transfer-circuitry isolation-voltage limit is set by a combination of the resistive-attenuator ratio, driver-signaling levels (related to the non-isolated and the isolated-supply voltages), differential-comparator common-mode range, and comparator signal-discrimination characteristics in the presence of noise. The specified limit for the MAX3250 is  $\pm 50V$  with an absolute maximum rating of  $\pm 80V$ . Internal back-to-back SCRs between logic and line circuits will break down when the limits are exceeded.

## Offset Isolation-Voltage and Frequency Considerations

The maximum applied offset voltage is dependent on frequency and the value of the power coupling capacitors (C1 and C2 in Figures 1 and 4). The dependence on C1 and C2 is due to a reverse pumping action caused by high levels of ground offset voltage. This means that there are different limits to  $V_{OS}$  when the circuit is powered by 3.3V or 5V supplies because C1 and C2 must be 470nF for 3.3V supply whereas 47nF is allowed for a 5V supply.

The isolated supply of Figure 4 is redrawn in **Figure 7** to include details of the square-pulse oscillator. Reverse charging paths are shown for  $V_{OS}$ -generated currents. When the  $V_{OS}$  polarity is as shown, a current, indicated by the solid line, will flow through Q2, C1, and D1 to charge C6. When the polarity is reversed, a current, indicated by the dashed line, will flow through D2, C2, and Q3 to charge logic-bypass capacitor C5.

 


Figure 7. Equivalent charge transfer circuit showing possible reverse pumping paths for  $V_{OS}$ .

The result of these reverse pump currents is insignificant for 5V logic operation when C1 and C2 are 47nF. No practical effect is seen for  $V_{OS} = \pm 50V$  even at 600Hz. A small ripple voltage may be observed on C6 at the higher frequencies. This is indicated by the flat curve in Figure 8 for 5V operation.

The results, however, are not insignificant for 3.3V operation when C1 and C2 are 470nF. As frequency and voltage are increased, ripple becomes increasingly apparent on C6. Eventually, ISO V+ is also affected. In extreme cases, ripple may begin to show on the logic supply at C5. The curve for 3.3V operation in **Figure 8** indicates the maximum applied isolation voltage vs. frequency for a 100ns jitter in received pulse width. This occurs when the modulation on C6 approaches 3Vpp. The maximum applied  $V_{OS}$  is  $\pm 50V$  at or below 80Hz, and decreases with frequency as shown. The curve will vary slightly with tolerance and temperature variations in the values of C1, C2, and C6 so this must be considered as a typical curve. Still, rather high levels of power-line harmonics can be tolerated.

 


Figure 8. Maximum applied offset voltage vs. frequency for 3.3V and 5V operation.

The capacitors selected for C1, C2, and C9 should be rated for 100V operation. Suitable surface-mount capacitors are: MuRata

GRM40X7R103K100 (10nF, 0805)  
GRM43X7R473K100 (47nF, 1808), and  
GRM44-1X7R474K100 (470nF, 2220), or equivalents.

Suitable radial-lead metalized film capacitors are: ITW Paktron

103K250RA2 (10nF, 250VDC)  
473K100RA2 (47nF, 100VDC), and  
474K100RA2 (470nF, 100VDC), or equivalents.

## Fail Safe

The RS-232 specification defines receiver differential thresholds as +3V and -3V. However, when a two-wire line is open circuited or when the line driver is not powered, the receive line signal voltage will be 0V, falling within the specified  $\pm 3V$  receiver threshold limits. To ensure a defined receiver state when this condition exists, the receiver input resistor pulls the receiver input voltage to ISO COM. As the receiver input low threshold is  $V_{IL} \geq 1V$ , a perceived zero input level (OFF condition) is assured per the RS-232 specification, thus ensuring that a connected UART does not recognize this as a start condition.

## Fault Signaling

A feature of the MAX3250 is a fault-condition flag output indicating when the device's isolation limit has been exceeded. The operation may be understood by reviewing the block schematic of Figure 1. Comparators on each side of the isolation barrier, F1a and F2, each compare a locally-generated reference voltage with the attenuated  $V_{CC}/2$  reference from the opposite side of the isolation barrier. References are chosen such that the attenuated equivalent of a 55V isolation voltage is recognized. One comparator recognizes a positive offset, and the other recognizes a negative offset. Outputs from the two comparators are logic ORed together to produce a fault signal whenever the difference between the logic common (GND) and ISO COM terminals exceeds  $\pm 55V$ .

## Protection Circuitry

There are two back-to-back 50V-breakdown SCR devices in series inside the IC to protect the circuitry if the voltage between ISO COM and logic-ground should exceed approximately  $\pm 100V$  either by accident or due to an ESD event. Specification limits for this voltage difference are  $\pm 80V$  due to potential inaccuracies in the SCR breakdown voltages. The continuous current into any of the isolated-side pins must be limited below 30mA to prevent latch-up when excess voltage is applied across the isolation barrier or after an ESD event when high applied isolation voltage is present. It is, therefore, advisable to insert a 1k $\Omega$  1/4W protective resistor in series with the test-voltage source when performing isolation-voltage tests. This, however, is unnecessary in normal applications where no more than  $\pm 50V$  (or the limits indicated in Figure 8) might be present.

There are internal SCR protection devices on each of the receiver inputs and transmitter outputs of the isolated side. Continuous voltage with respect to ISO COM on  $R_{IN1}$  and  $R_{IN2}$  must be limited to  $\pm 25V$ . Continuous voltage on  $T_{OUT1}$  and  $T_{OUT2}$  with respect to ISO COM must be limited to  $\pm 13.2V$ . These are low-current protective devices that must not be subjected to continuous currents in excess of 30mA.

NOTE: A 1k $\Omega$  resistor need not be placed in series with the ISO COM line in normal applications as was indicated in Revision 0 of the MAX3250 data sheet dated 4/02. In fact, the addition of the 1k $\Omega$  resistor will cause received data errors. Revision 1 of the data sheet omits this suggestion.

## Conclusion

By utilizing a resistive-isolation technique and capacitive voltage transfer to power the isolated circuits, the MAX3250 functions as a low-cost replacement for capacitively-, optically-, or magnetically-isolated transceivers in the majority of systems requiring moderate isolation-voltage capability. Its several other useful features are adequately described in the data sheet.

## Notes

<sup>1</sup> TIA-EIA STANDARD, Interface Between Data Terminal Equipment and Data Circuit-Terminating Equipment Employing Serial Binary Data Interchange, Rev. F, ANSI/TIA/EIA-232-F-1997, 30 September 1997.

### Related Parts

<a href="#">MAX3250</a>	±50V Isolated, 3.0V to 5.5V, 250kbps, 2 Tx/2 Rx, RS-232 Transceiver	<a href="#">Free Samples</a>
-------------------------	---	------------------------------

---

### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 1846: <http://www.maximintegrated.com/an1846>

APPLICATION NOTE 1846, AN1846, AN 1846, APP1846, Appnote1846, Appnote 1846

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>