



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Amplifier and Comparator Circuits](#) > APP 1860

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Automotive](#) > APP 1860

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Sensors](#) > APP 1860

Keywords: silicon piezoresistive sensors, PRTs, pressure-sensing applications, Wheatstone Bridge, sensor-signal conditioners, ratiometric output, current-loop output

TUTORIAL 1860

# PWM Outputs Enhance Sensor Signal Conditioners

Jan 24, 2003

*Abstract: This application note explains that piezoresistive sensors have nonlinear error over temperature. This error can be reduced to within 1% of the sensor's inherent repeatability limitations by using a Maxim sensor signal conditioner and transmitter to transmit sensor information. One transmission method modulates the ratiometric output using pulse-width modulation (PWM). Like its current-loop counterpart, the PWM output has good noise immunity and is suitable for transmission over longer distances. The MAX1452 sensor signal conditioner is featured.*

A similar version of this article appeared in the March 2002 issue of *Medical Design News* magazine.

## Introduction

Most of today's silicon piezoresistive sensors are used in pressure-sensing applications. Fabricated using bulk micro-machining techniques, they are usually arranged as a four-resistor Wheatstone bridge on a single monolithic die. Like integrated circuits, the sensors are inexpensive because they are processed on a wafer containing hundreds to several thousands of sensing elements. Thus far, most of these IC sensors are used for the low- to medium-accuracy requirements of automotive, consumer, and industrial applications.

Piezoresistive sensors are known to have nonlinear error over temperature, which has limited their use in the higher-end markets currently addressed by more costly strain gauges and other sensor types. Correcting the complex errors of a silicon piezoresistive sensor normally requires a considerable amount of electronics, but sensor signal conditioners from Maxim (the [MAX1450](#), [MAX1452](#), [MAX1455](#), [MAX1462](#), and [MAX1464](#)) correct these errors to within 1% of the sensor's inherent repeatability limitations. Maxim's sensor signal conditioners create inexpensive transducers, providing total errors < 1% over a wide operating temperature range.

## Benefits of a Current-Loop Transducer

The most common transducer outputs are the ratiometric output (0.5V to 4.5V) and the current-loop output (4mA to 20mA). A standard ratiometric circuit compensates the sensor over the entire temperature range, to an offset of 0.5V and a span of 4.0V. Current loops, for which the desired offset is 4mA and the desired span is 16mA, offer several advantages over the voltage-output transducer.

Current loops do not require precise and stable supply voltages; their insensitivity to  $V = IR$  drops makes them suitable for long-distance transmission; and the 2-wire twisted pair commonly used for current loops offers very good noise immunity. Power is furnished remotely, through the 4mA of current not needed for information transfer. The 4mA offset also provides a distinction between zero (4mA) and no information (no current flow).

## Pulse-Width Modulation (PWM) Offers Better Operating Efficiency

Another way to transmit sensor information is to modulate the ratiometric output using pulse-width modulation (PWM). The modulating signal ( $V_M$ ) is the transducer's ratiometric output. In a PWM configuration the desired offset corresponds to a 10% duty cycle and the span corresponds to an 80% duty cycle. As the sensor's ratiometric output changes from 0.5V to 4.5V, the corresponding duty cycle changes from 10% to 90%. Like its current-loop counterpart, the PWM output has good noise immunity and is suitable for transmission over longer distances.

PWM provides better operating efficiency in battery-powered applications. In a 5V system the current-loop transducer requires 20mW to 100mW for information transfer. Transmitting the ratio metric output with PWM will require less than 1mW when the PWM transmitter is connected to a high-impedance node.

The simplest way to generate a PWM signal is to compare the message signal to a triangular or ramp waveform. The resulting output is high when the input is greater than the triangular waveform (the carrier), and low when the input is less (**Figure 1**). Thus, the two basic blocks required for PWM are a triangular-waveform generator and a comparator.

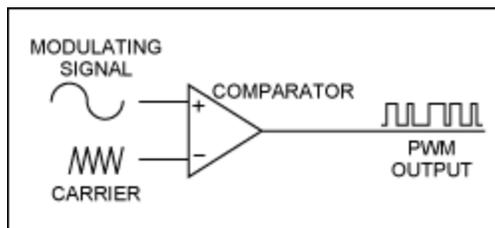


Figure 1. A comparator configured as shown produces a PWM output.

In **Figure 2**, the [MAX492](#) op amp generates the triangular waveform and the [MAX942](#) comparator produces the PWM output signal. Waveforms from this circuit and the relevant equations are shown in **Figure 3**.

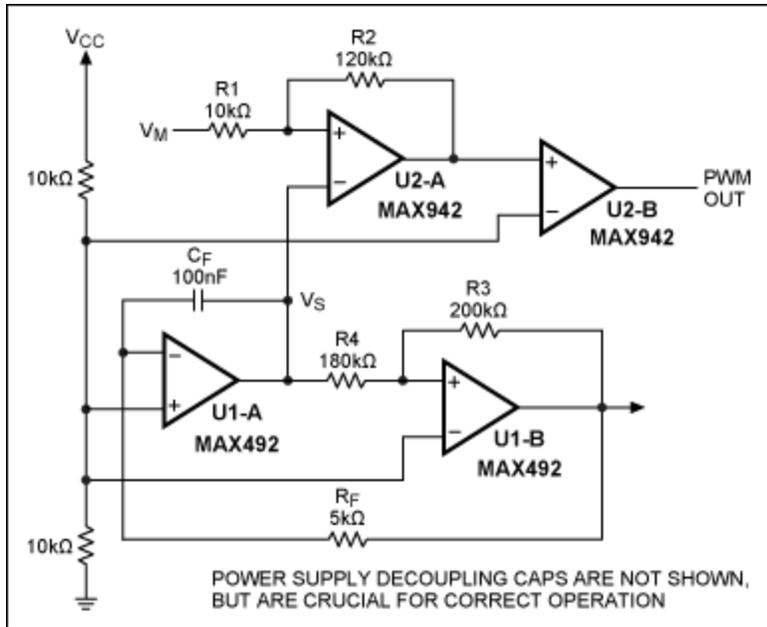


Figure 2. The triangular wave in this basic configuration is produced by a dual op amp (U1). The PWM signal is produced by a dual comparator (U2).

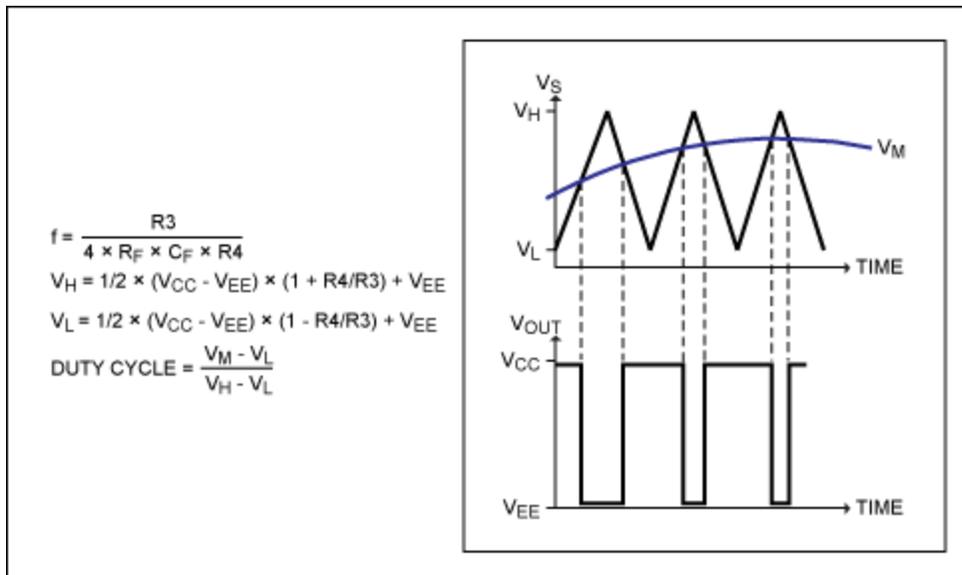


Figure 3. These waveforms and equations illustrate operation of the circuit in Figure 2.

The MAX492 dual rail-to-rail op amp generates the triangular wave. Rail-to-rail capability is required because the dynamic range of the triangular waveform must be larger than that of the sensor. The integrator circuit (U1-A) generates a positive- or negative-going ramp with slope determined by  $R_F$  and  $C_F$ . The comparator stage (U1-B) reverses the slope of the ramp, and the triangular-waveform frequency is given by the equation in Figure 3. For the component values shown, the ramp frequency and thus the PWM output is about 500Hz. Though not shown in Figure 2 and **Figure 4**,  $0.1\mu\text{F}$  decoupling capacitors should be included at the supply terminals.

A dual comparator (the MAX942) compares the ramp waveform with the sensor's analog voltage. This



measure the PWM output for minimum pressure (PWM0). The PWM span is then  $PWMSpanT1 = PWMFS - PWM0$ . Because the required span is normally 80%, the needed span DAC value can be calculated using the expression:

$$IdealSpanDACT1 = CurrentSpanDAC \times 80\%/PWMSpanT1$$

The offset DAC is then set to obtain an output with 10% duty cycle.

To obtain values for the span and offset DACs, repeat the above procedure with the transducer at temperature T2. You can add more temperature points (up to 114) for higher accuracy. Programming up to 114 independent 16-bit EEPROM locations enables correction in 1.5°C increments over the -40°C to +125°C temperature range. (Correction coefficients loaded into the lookup table are linear interpolations between the values recorded for each DAC at each temperature.) Multipoint capability not only enables a simple first-order sensor compensation, but it lets you match unusual temperature curves as well. Following this procedure for the above circuit compensates the sensor quickly, efficiently, and within 0.2% of its inherent repeatability error.

#### Related Parts

<a href="#">MAX1450</a>	Low-Cost, 1%-Accurate Signal Conditioner for Piezoresistive Sensors	
<a href="#">MAX1452</a>	Low-Cost Precision Sensor Signal Conditioner	<a href="#">Free Samples</a>
<a href="#">MAX1455</a>	Low-Cost Automotive Sensor Signal Conditioner	<a href="#">Free Samples</a>
<a href="#">MAX1462</a>	Low-Voltage, Low-Power, 16-Bit Smart ADC	
<a href="#">MAX1464</a>	Low-Power, Low-Noise Multichannel Sensor Signal Processor	<a href="#">Free Samples</a>

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1860: <http://www.maximintegrated.com/an1860>

TUTORIAL 1860, AN1860, AN 1860, APP1860, Appnote1860, Appnote 1860

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>