

Keywords: current sensor, negative supply, current sense amplifier, negative current monitor, current sense amp, current monitor

## APPLICATION NOTE 2011

# High-Side Positive Current Sensor Monitors Negative Supply

Jun 20, 2003

*Abstract: This application note uses a high-side current-sense amplifier to monitor the current from a negative supply voltage. The circuit uses the IC's wide common-mode input range to amplify a small Vsense signal at the negative supply and level shift it up to a positive output voltage.*

All dedicated current-sense amplifiers are designed for high-side sensing on a positive supply, but you can adapt them to monitor a negative supply (**Figure 1**). The positive supply pin (V+) connects to the system's positive supply, and the ground pin (GND) connects to the negative supply (V<sub>EE</sub>). That arrangement monitors the negative supply while providing a positive output voltage for the external interface (typically an A/D converter). The RS+ pin of the current-sense amplifier (U1) connects to the load, and the RS- pin connects to the negative supply.

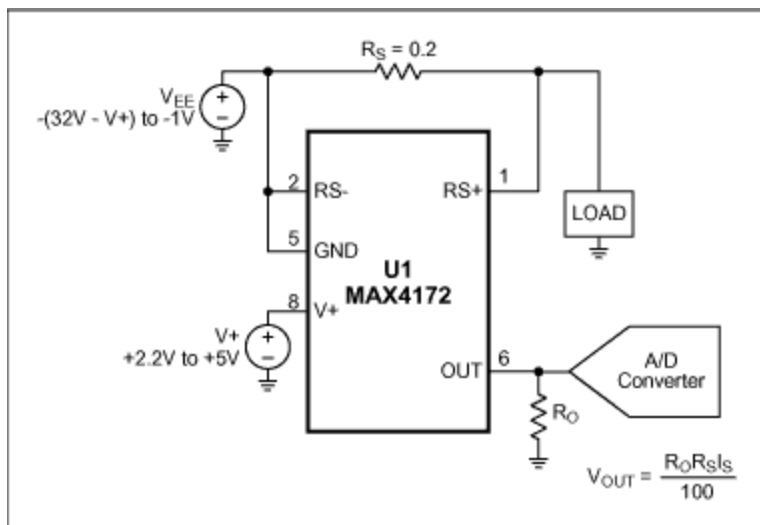


Figure 1. Connecting this positive-supply-current monitor (U1) as shown lets it monitor a negative current while generating a positive output voltage for the ADC.

U1's current-source output drives a current that is proportional to load current flowing to ground (not to the GND pin). Output resistor R<sub>O</sub> converts the current to a voltage, which is then digitized by an ADC

(optional):

$$V_{OUT} = \frac{R_O R_S I_S}{100}$$

The maximum output voltage is limited by saturation in the internal transistors (which occurs at approximately  $V_+ - 1.2V$ ). Thus,  $V_+$  must exceed the full-scale output by at least 1.2V. If, for instance, the full-scale output is 1V, then  $V_+ \geq +2.2V$ . To meet the device's maximum and minimum operating voltages,  $0 \geq V_{EE} \geq -(32 - V_+)$  and  $(V_+ - V_{EE}) \geq +3V$ . **Figure 2** shows the variation of current-measurement accuracy with load current.

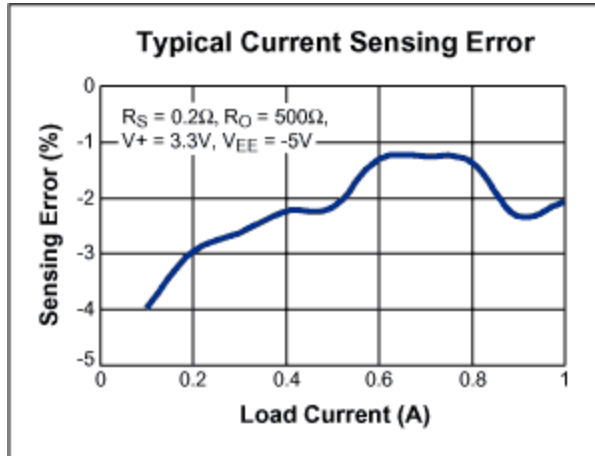


Figure 2. The Figure 1 current-sensing error varies with load current as shown.

#### Related Parts

[MAX4172](#)

Low-Cost, Precision, High-Side Current-Sense Amplifier

[Free Samples](#)

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 2011: <http://www.maximintegrated.com/an2011>

APPLICATION NOTE 2011, AN2011, AN 2011, APP2011, Appnote2011, Appnote 2011

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>