



Maxim > Design Support > Technical Documents > Application Notes > Automotive > APP 2768

Keywords: ASK receiver, tire pressure monitoring system, TPMS, low-frequency RF, LFRF, LFRF receiver

## APPLICATION NOTE 2768

# Ultra-Low Quiescent Supply Current 125kHz ASK Receiver

Oct 01, 2003

**Abstract:** This application note shows a simple design for a 125kHz ASK receiver for a tire pressure monitoring system (TPMS). This LFRF receiver needs only a 2.1V supply voltage and 4 $\mu$ A (typ) supply current. The design uses a tiny comparator acting as a limiting amplifier, the MAX9075, and a transistor for detection. A nanopower comparator, the MAX9117, can be used to reduce the supply current to 600nA (typ).

There is an emerging automotive market: Tire Pressure Monitoring Systems (TPMS). These systems, which will soon be mandated for new cars, monitor the tire pressure and alert the driver when pressure is outside specifications. Proper tire pressure enhances fuel economy and vehicle safety.

Powering these systems is a complex challenge. Components are built into the wheel, so the batteries used must be light in weight. Batteries must offer a seven-year life, as they are permanently molded into the modules and cannot be replaced.

Because of the difficulty in providing a connection between the vehicle and a rotating wheel, wireless systems are a common solution. Pressure information is transmitted via a RF channel at a frequency that varies with the country (usually, 315MHz, 434MHz or 868MHz). Transmitters are generally switched on and off, to prevent excess interference and prolong battery life.

Some systems use a mechanical switch and others use an algorithm, which cycles the transmitter based on rotation speed. Many designs use a LFRF (low-frequency RF) solution: a 125kHz magnetic field wakes up the tire-mounted TPMS module, which transmits the pressure-related signal and returns to sleep mode. The module is controlled by electronics on the vehicle. The TPMS module needs a LFRF receiver with very low power consumption.

This application note describes an ASK receiver at 125kHz with a 2.1V supply voltage requirement and only 4 $\mu$ A typical supply current when there is no LFRF trigger signal. Sensitivity is adjustable and is typically around 5mVp-p. The design is based on the best speed/consumption comparator on the market: the **MAX9075**. It is available in a tiny SC70 package

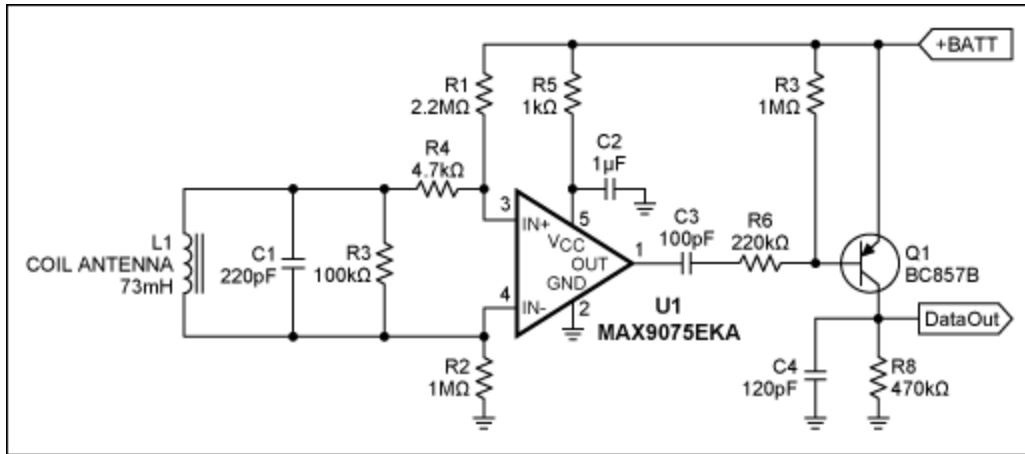


Figure 1.

The antenna is a coil, tuned with a fixed or adjustable capacitor. The loaded Q factor is set by R3 and can be 10 or more, depending on the accuracy of the coil and the capacitors and the desired data rate.

The MAX9075 acts as a limiting amplifier. A single transistor, Q1, is used for detection. The values of the detector section are adjusted according to the desired data rate.


R1 and R2 form the bias resistor network. The bias current is about  $1\mu\text{A}$  with a new lithium battery ( $\approx 3.2\text{V}$ ). R4 generates an offset to adjust the sensitivity. If  $R4 = 0$ , sensitivity is optimum but there is a risk of oscillation because the MAX9075 has no internal hysteresis. In this case, the real sensitivity is unknown because it depends upon internal offset. It is typically  $\pm 1\text{mV}$  but the maximum is  $\pm 8\text{mV}$ .

According to the global offset, the output state of the comparator is unknown. C3 eliminates the "DC level." In this example, the detector transistor is a PNP, and the demodulated output is positive.  $\text{DataOut} \approx \text{VCC}$  if LF signal is present, and  $\text{DataOut} \approx 0\text{V}$  without the LFRF input signal.

R5/C2 is the power supply filter. It has about a 1ms rise time (cycling mode).

If a high magnetic field can be applied at the antenna, a dual diode, such as the BAV99, is necessary between pins 3 and 4 of U1, to limit the peak/peak voltage applied to the comparator's inputs. In TPMS systems, the dynamic range of the input signal is not very high because the distance between the emitting coil and the TPMS module is fairly constant.

An optional nanopower comparator, such as the **MAX9117** in SC70, can be used to ensure a good square output waveform (see **Figure 2**). Its supply current is only  $600\text{nA}$  typical at  $1.8\text{V}$  and it integrates a voltage reference internally connecting to IN- (pin4) which is AC decoupled with  $C5 = 1\text{nF}$ .

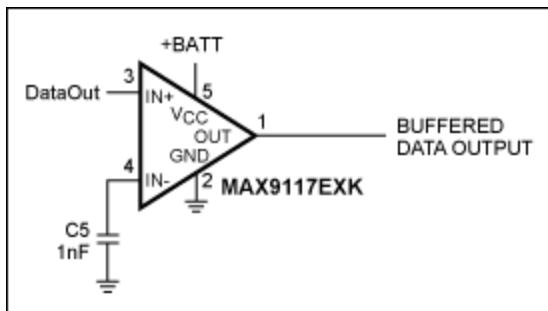

*Figure 2.*

Related Parts		
MAX9075	Low-Cost, Ultra-Small, 3µA Single-Supply Comparators	Free Samples
MAX9117	SC70, 1.6V, Nanopower, Beyond-the-Rails Comparators With/Without Reference	Free Samples

---

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 2768: <http://www.maximintegrated.com/an2768>

APPLICATION NOTE 2768, AN2768, AN 2768, APP2768, Appnote2768, Appnote 2768

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>