

Keywords: positive emitter-coupled logic, PECL, low-dropout regulators, LDO, line termination, linear regulators

## APPLICATION NOTE 3198

# Modified LDO Sinks PECL-Termination Current

Jun 23, 2004

*Abstract: By configuring a current-sinking negative LDO to operate as a positive-voltage sink, you can construct a low-voltage supply (1.3V) for terminating PECL-logic lines.*

Also See: [Modified LDO Regulator Sinks PECL-Termination Current](#)

The positive emitter-coupled logic (PECL) used in high-speed telecommunications requires odd supply voltages: a positive  $V_{CC}$  of +3.3V, and a termination voltage ( $V_{TT}$ ) equal to  $V_{CC} - 2V = +1.3V$ . The  $V_{TT}$  supply is regulated with respect to  $V_{CC}$ , and must be able to sink current.

Most positive low-dropout (LDO) regulators cannot sink current. Negative LDOs are designed for that purpose but normally deliver a negative voltage.

**Figure 1** shows a current-sinking negative LDO modified for positive-voltage operation. The GND pin connects to  $V_{CC}$ , and IN connects to ground. Those connections allow the negative LDO to operate as a positive-voltage sink in which the voltage at  $V_{SET}$  equals  $V_{CC} - 1.25V$ :

$$V_{SET} = V_{CC} - 1.25V$$

$$V_{CC} - V_{SET} = 1.25V$$

$$\frac{(V_{CC} - V_{OUT})}{R_1 + R_2} R_2 = 1.25V$$

$$V_{OUT} = V_{CC} - (R_1 + R_2) \left( \frac{1.25V}{R_2} \right)$$

$$V_{OUT} = V_{TT} = V_{CC} - 2V \quad (\text{FOR PECL})$$

$$(R_1 + R_2) \left( \frac{1.25V}{R_2} \right) = 2V \quad (\text{FOR PECL})$$

$$R_1 = 0.6R_2 \quad (\text{FOR PECL})$$

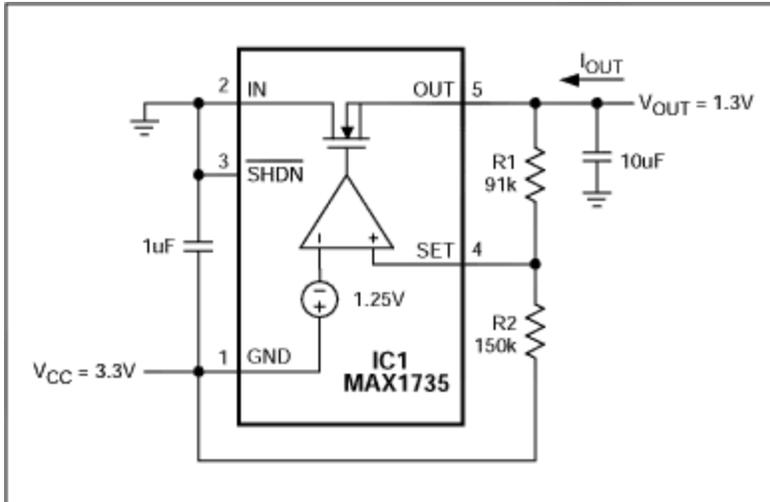


Figure 1. The connections shown enable a negative-output LDO (with its inherent current-sinking ability) to generate a positive output voltage.

The output voltage is regulated with respect to  $V_{CC}$ . That feature is perfect for PECL-termination applications, because it requires the output voltage to track the  $V_{CC}$  supply. Maximum output current is limited by the internal protection circuitry (to about 400mA) and by the package power-dissipation rating (about 550mW). For applications that require higher output voltage or higher current (or both), you can add series diodes to dissipate some of the power (**Figure 2**). You can add as many diodes as needed to dissipate power, but the voltage at OUT (Pin 5) must remain at least 300mV above ground (IN, pin 2).

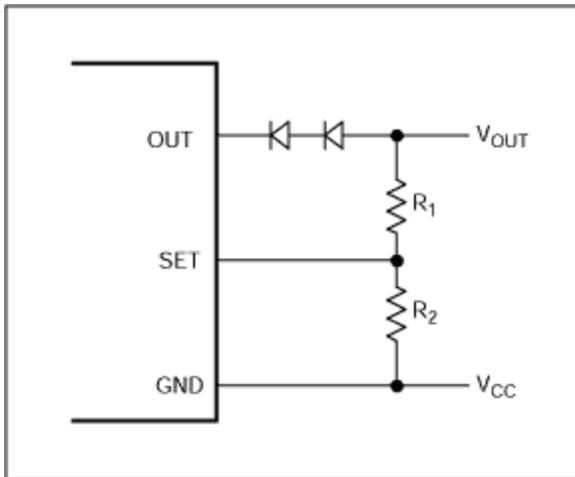


Figure 2. To operate the Figure 1 circuit at a voltage or current that would otherwise exceed IC1's internal or package power-dissipation ratings, add power-dissipating diodes as shown.

#### Related Parts

[MAX1735](#)

200mA, Negative-Output, Low-Dropout Linear Regulator in SOT23

[Free Samples](#)

---

**More Information**

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 3198: <http://www.maximintegrated.com/an3198>

APPLICATION NOTE 3198, AN3198, AN 3198, APP3198, Appnote3198, Appnote 3198

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>