

Keywords: pulse-width modulation, PWM, pulse width modulator, integrator, comparator, triangle-wave generator

#### APPLICATION NOTE 3201

# Pulse-Width Modulator Operates at Various Levels of Frequency and Power

Jun 23, 2004

*Abstract: Build a general-purpose pulse-width modulator using three op amps from a quad-op-amp device.*

The many applications for pulse-width modulation (PWM) include voltage regulation, power-level control, and fan-speed control. A PWM circuit for such applications (**Figure 1**) can be implemented with three op amps from a single quad-op-amp chip. The use of op amps allows a wide variety of applications. Low-power op amps can be used in a low-power system, for example, and high-frequency op amps can be used for a high-frequency PWM. The Figure 1 circuit also generates a triangular wave.

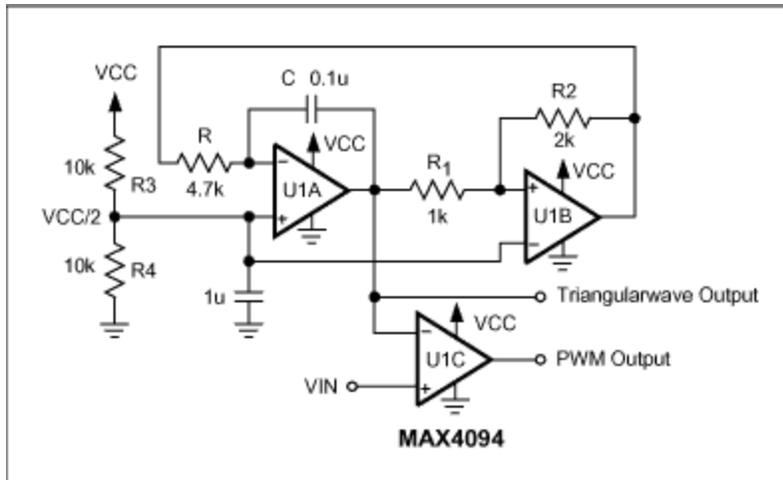


Figure 1. This 3-op-amp circuit produces a triangular wave and a variable-pulsewidth output.

The circuit consists of a triangle-wave generator (U1A and U1B) and a comparator (U1C). U1A is configured as an integrator (or de-integrator), and U1B as a comparator with hysteresis. At power-up, the comparator's output voltage is assumed to be zero.

U1A's non-inverting input is biased at  $V_{CC}/2$ . A virtual connection between the inverting and non-inverting inputs allows a constant current through R equal to  $I = V_{CC}/2R$ , which charges the capacitor C. Thus, the U1A integrator output increases linearly with time. When it reaches  $0.75V_{CC}$ , the comparator output (U1B) changes to its maximum output voltage ( $V_{CC}$ ). At that point the integrator begins to de-

integrate, causing the output voltage to decrease linearly. When it reaches  $0.25V_{CC}$  the comparator output voltage changes to zero, and the cycle repeats. Thus, the integrator output is a triangular wave that swings between the levels of  $\frac{1}{4} V_{CC}$  and  $\frac{3}{4}V_{CC}$ .

U1C compares the triangular wave against the dc level  $V_{IN}$ . Its output is a square wave, with a duty cycle that varies from 0% to 100% as  $V_{IN}$  varies from  $\frac{1}{4} V_{CC}$  to  $\frac{3}{4} V_{CC}$  (**Figure 2**). Frequency is determined by  $R$ ,  $C$ ,  $R_1$ , and  $R_2$ :

$$f = \frac{R_2}{4RCR_1}, \text{ where } R_2 > R_1.$$

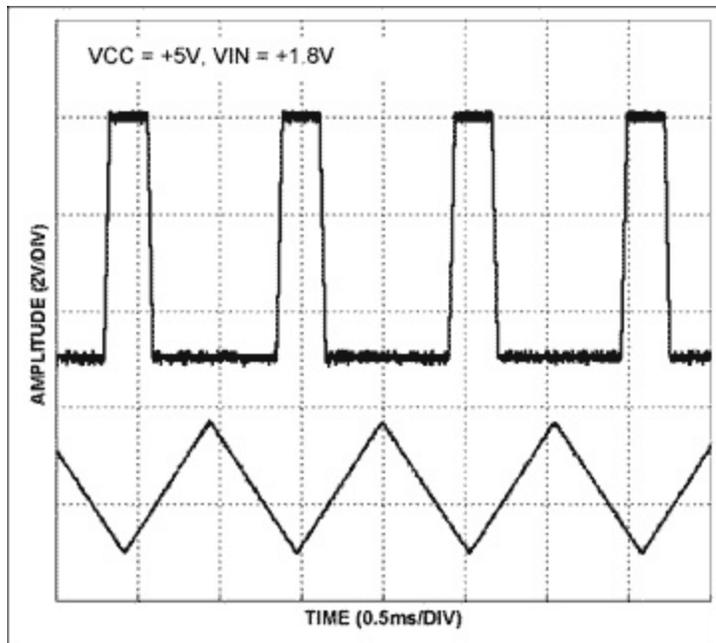


Figure 2. The Figure 1 circuit produces these PWM and triangular-wave outputs.

The ratio of  $R_2$  and  $R_1$  affects the operating frequency and the amplitude of the triangular wave. Given that  $V_{TH}$  is the triangular wave's maximum voltage and  $V_{TL}$  is its minimum voltage, the amplitude swing is:

$$V_{TH} = \frac{V_{CC}(R_1 + R_2)}{2R_2} \text{ and } V_{TL} = \frac{V_{CC}(R_2 - R_1)}{2R_2}, \text{ where } R_2 > R_1.$$

$$\text{Therefore, } V_{TH} - V_{TL} = \frac{R_1}{R_2} V_{CC} \text{ (} R_2 > R_1 \text{)}.$$

The triangular wave's peak-to-peak voltage (the difference in its maximum and minimum voltages) is centered at the  $V_{CC}/2$  bias voltage generated by  $R_3$  and  $R_4$ . The circuit configuration shown allows the PWM to operate on a single supply. Use micropower op amps and larger resistors ( $R$  and  $R_1 - R_4$ ) for low-power applications, and high-frequency op amps for higher-frequency applications. (The quad op amp shown comes in a single package.)

#### Related Parts

[MAX4094](#)

Single/Dual/Quad, Micropower, Single-Supply, Rail-to-

[Free Samples](#)

---

**More Information**

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 3201: <http://www.maximintegrated.com/an3201>

APPLICATION NOTE 3201, AN3201, AN 3201, APP3201, Appnote3201, Appnote 3201

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>