



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Amplifier and Comparator Circuits](#) > APP 3330  
[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Power-Supply Circuits](#) > APP 3330

Keywords: charge pumps, regulated charge pumps, quiescent current, portable devices, comparators

#### APPLICATION NOTE 3330

# Build a Charge Pump with Ultra-Low Quiescent Current ( $I_q$ )

By: Greg Sutterlin  
Sep 24, 2004

*Abstract: Combining low-on-resistance analog switches with a reference and ultra-low quiescent current comparator produces a discrete-component regulated charge pump that delivers 10mA, with only 7 $\mu$ A of quiescent current ( $I_q$ ).*

Portable, battery-powered devices often spend most of their life in standby mode, where the quiescent current of an internal boost converter bleeds the battery continuously. The quiescent current during standby can be larger than the actual load current. Though several inductor-based converters offer amazingly low quiescent current (<10 $\mu$ A maximum), a regulated charge pump is preferred (or required) for cost-sensitive designs that must be intrinsically safe.

Off-the-shelf regulated charge pumps with output-current capabilities  $\geq 10$ mA have typical minimum quiescent currents of 50 to 100 $\mu$ A. If that level of quiescent current is not acceptable, you can reduce the overall average by adding circuitry that monitors the regulated voltage remotely and toggles the charge pump in and out of shutdown. That approach, however, may not achieve the desirable  $I_q$  level (<10 $\mu$ A). The advent of low- $R_{ON}$  analog switches and ultra-low-current comparators and references makes possible a discrete-component charge pump whose maximum quiescent current is about 7 $\mu$ A.

Charge pumps use an ac-coupling technique to transfer energy from a transfer capacitor to a storage capacitor. The transfer capacitor is first charged via analog switches to the level of  $V_{BATT}$ , then other analog switches transfer the energy to a storage capacitor tied to  $V_{OUT}$ . The transfer capacitor is then charged again and the cycle repeats. With ideal analog switches exhibiting zero loss, the  $V_{OUT}$  level equals  $2V_{BATT}$ . As expected, however, the analog switches' finite  $R_{ON}$  produces an output level that drops in proportion to the load current.

A basic regulated charge pump (**Figure 1**) includes an oscillator, several analog switches, a voltage reference, and a comparator. The comparator serves as a voltage monitor and oscillator. When the circuit is in regulation the comparator output is low, which closes the NC switches and allows C1 to charge to  $V_{BATT}$ . When the voltage at  $V_{OUT}$  dips below the output-regulation threshold (3.3V in this case), the comparator output goes high. The NO switches close, transferring C1's charge to C2. This cycle repeats until  $V_{OUT}$  regains regulation.

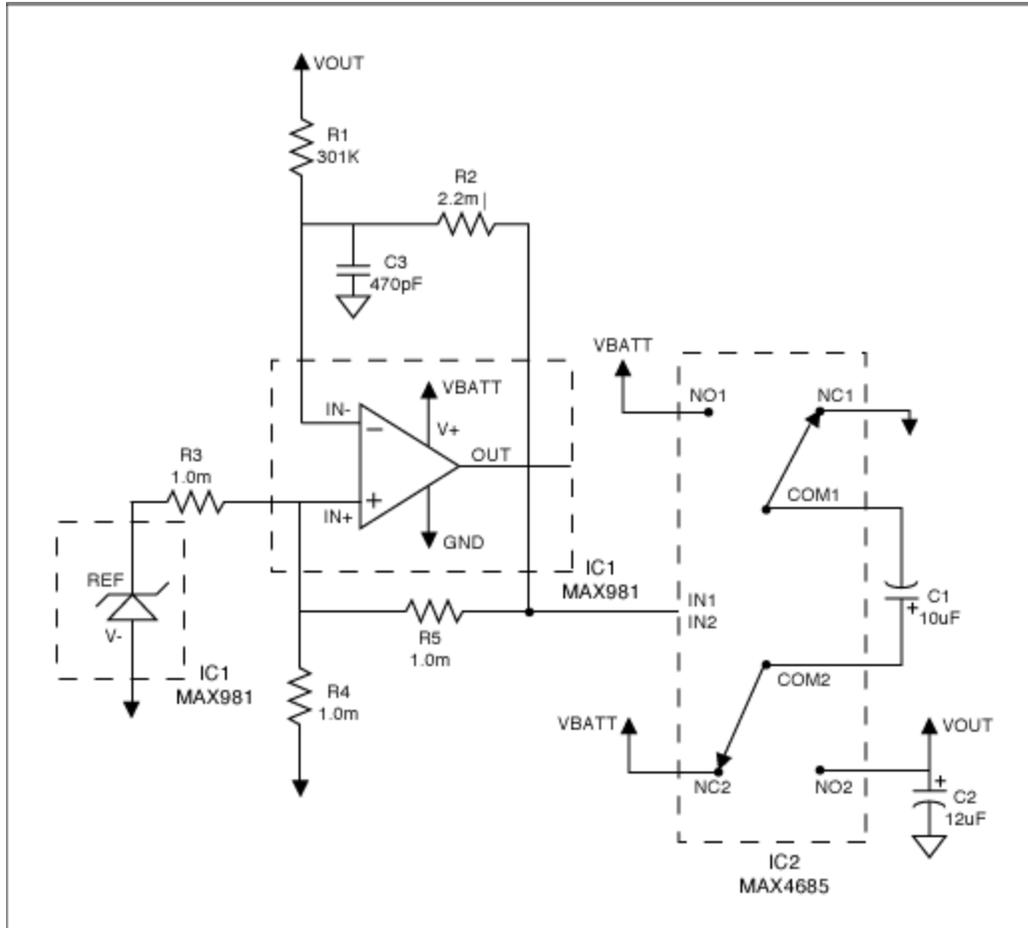


Figure 1. Low-Iq regulated charge pump.

Resistors R3-R5 form the hysteresis necessary for oscillation. Their value (1.0M $\Omega$ ) creates a notable level of hysteresis while minimizing  $V_{BATT}$  loading. As the comparator output changes state, feedback resistor R5 creates hysteresis by moving the threshold applied to the comparator's IN+ input. For the resistor values shown, reference value nominal for IC1 (1.182V), and  $V_{BATT} = 3.0V$ , the  $V_{IN+}$  threshold swings between approximate values of  $V_{IN+low} = 0.39V$  and  $V_{IN+high} = 1.39V$ .

When the circuit is in regulation,  $V_{IN-}$  slightly exceeds  $V_{IN+}$ , the comparator output is low, the voltage at  $V_{OUT}$  is sensed by the R1/R2 divider, and the threshold at  $V_{IN+}$  is low (0.39V). With  $V_{IN+}$  at 0.39V, the R1 and R2 values can be calculated from the following equation:

$$V_{IN+} = V_{OUT}(R2/(R1+ R2)).$$

The magnitude of R1+R2 should be greater than 1M $\Omega$  to minimize  $V_{BATT}$  loading. If  $V_{OUT} = 3.3V$  and R2 is selected at 2.2M $\Omega$ , R1 is calculated at 301k $\Omega$ . Capacitor C3 connects to the comparator's IN- input. Along with R1 and R2, C3 sets the oscillation frequency according to the following simplified relationships:

$$t_{discharge} = t_{low} = -R2 \cdot C3 \cdot \ln(V_{IN+low}/V_{IN+high}).$$

$$t_{charge} = t_{high} = -R2 \cdot C3 \cdot \ln(1 - ((V_{IN+high} - V_{IN+low}) / (V_{BATT} - V_{IN+low}))).$$

$f_{osc} = 1/t_{period}$ , where  $t_{period} = t_{low} + t_{high}$ .

To maximize efficiency and reduce the effects of comparator slew rate, you should set a relatively low frequency. Choosing  $C3 = 470\text{pF}$  yields the following:

$t_{low} = 178\mu\text{sec}$  and  $t_{high} = 68\mu\text{sec}$ ; thus  $f_{osc} = 4.0\text{kHz}$ .

The values of  $C1$  and  $C2$  are selected to achieve the desired load current and ripple. For this application ( $I_{load} = 10\text{mA}$ ), choose  $C1 = 10\mu\text{F}$ . To calculate the value of  $C2$ , make an approximation based on the desired ripple voltage:

$C2 = (I_{load} * t_{low})/V_{ripple}$ .

With  $I_{load} = 10\text{mA}$  and  $V_{ripple} = 150\text{mV}$ ,  $C2 = 12\mu\text{F}$ .

With the component values shown, the circuit draws a maximum  $I_q$  of  $6.9\mu\text{A}$  and offers a considerable improvement over off-the-shelf charge pumps. You can further lower the  $I_q$  value by increasing the resistor values, but that effect is minimal because IC2's quiescent current ( $3.8\mu\text{A}$  maximum) dominates the total. This circuit lets you implement an ultra-low- $I_q$  regulated charge pump. Until off-the-shelf options are available, it provides an alternative for designers seeking to implement a low-cost design without the use of inductors.

This design idea appeared in the August 5, 2004 issue of *EDN* magazine.

#### Related Parts

<a href="#">MAX4685</a>	0.5Ω/0.8Ω Low-Voltage, Dual SPDT Analog Switches in UCSP	<a href="#">Free Samples</a>
<a href="#">MAX985</a>	Micropower, Low-Voltage, UCSP/SC70, Rail-to-Rail I/O Comparators	<a href="#">Free Samples</a>

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 3330: <http://www.maximintegrated.com/an3330>

APPLICATION NOTE 3330, AN3330, AN 3330, APP3330, Appnote3330, Appnote 3330

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>