

Keywords: shunt regulator, current limit, power amplifier, adjustable shunt regulator


## APPLICATION NOTE 3867

# Shunt Regulator Improves PA's Current-Limit Accuracy

Jul 26, 2006

*Abstract: Substituting a shunt regulator (U1) for the usual transistor in this power-amplifier circuit improves the current-limit accuracy.*

Adding current-limiting circuitry to an emitter follower protects both the pass transistor and downstream circuitry from excessive current damage. The classic way to implement such current limiting is to add a ballast resistor between the pass transistor's emitter and the circuit output, and then monitor the resistor drop with a small-signal transistor. See R4 and Q2 in the power amplifier (or linear regulator) shown in **Figure 1**.

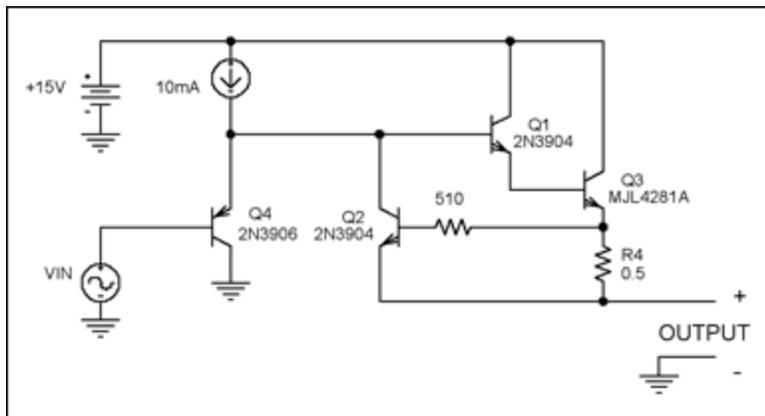

*Figure 1. A small-signal transistor (Q2) provides an output current limit for this power amplifier.*

Unfortunately, the base-emitter voltage of the small-signal transistor sets the current-limit threshold for this circuit. That  $V_{BE}$  has a well-known temperature coefficient of  $-2\text{mV}/^\circ\text{C}$ , which causes a substantial change in current limit across the operating temperature range.

An adjustable shunt regulator (U1 in **Figure 2**) is preferable to the small-signal transistor for sensing current. This IC is chosen for its low-input threshold (0.6V), which is lower than that of common shunt regulators (1.25V to 2.5V). In addition, the IC's separate power-supply input allows it to maintain accuracy as the internal output transistor approaches saturation.

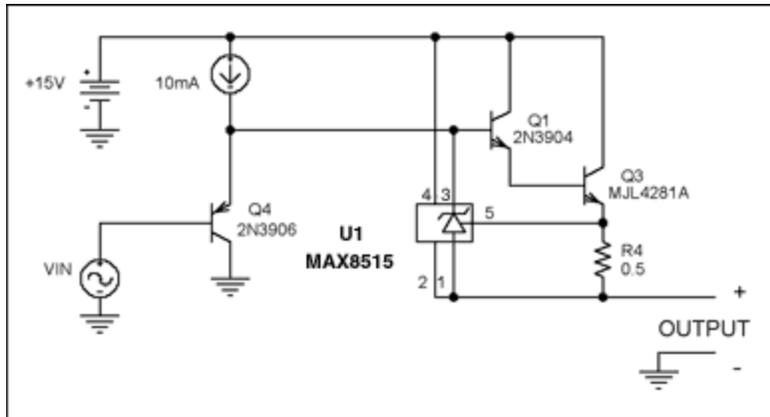


Figure 2. Substituting a shunt regulator (U1) for Q2 in the Figure 1 circuit improves the current-limit accuracy.

Figure 3 compares current-limit accuracies of the small-signal-transistor version of Figure 1 with the shunt-regulator version of Figure 2. The transistor version exhibits a 25% change in current-limit threshold over the operating temperature range, while the shunt-regulator provides better than 2% accuracy over that range (neglecting the temperature coefficients of the sense resistors).

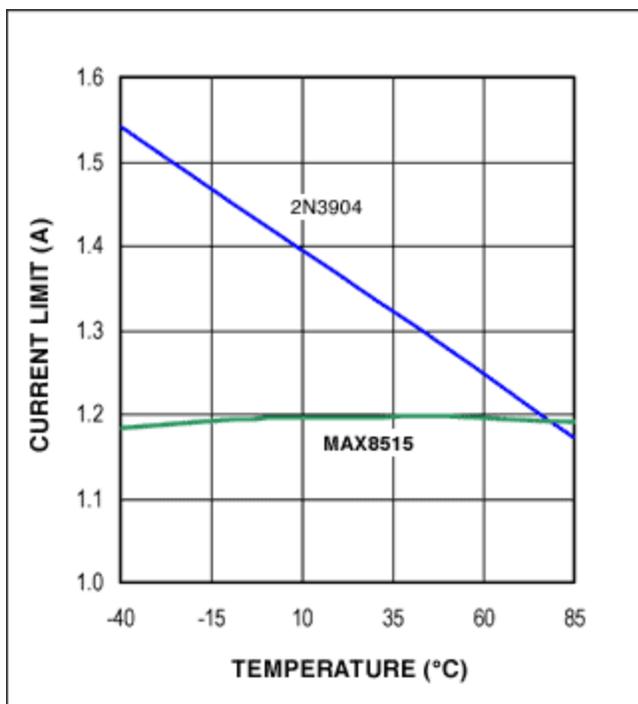


Figure 3. Current-limit accuracy versus temperature for the circuits of Figure 1 (top trace) and Figure 2 (bottom trace).

A similar article appeared as a Design Idea in the February 2, 2006 edition of *EDN*.

#### Related Parts

[MAX8515](#)

Wide-Input 0.6V Shunt Regulators for Isolated DC-DC Converters

[Free Samples](#)

---

**More Information**

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 3867: <http://www.maximintegrated.com/an3867>

APPLICATION NOTE 3867, AN3867, AN 3867, APP3867, Appnote3867, Appnote 3867

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>