



This circuit includes a constant-frequency, current-mode step-up converter (U1, the [MAX1896](#)) with suitable current limiting. The step-up converter creates the +12V output; an external charge pump consisting of D1, D2, C1, and C2 generates the negative rail.

The circuit can source or sink about 50mA, and the MAX1896's current-mode topology limits the switch current on a cycle-by-cycle basis. Note that the MAX1896's internal switch is not in series with the current path, so it cannot limit current when the output voltage is forced below the input-supply voltage. Thus, a dead short is limited only by the USB current-limit fuse, which is usually rated much higher than 500mA. Load regulation for the +12V output is shown in the MAX1896 data sheet. For the -12V output, load regulation is shown in **Figure 2**.

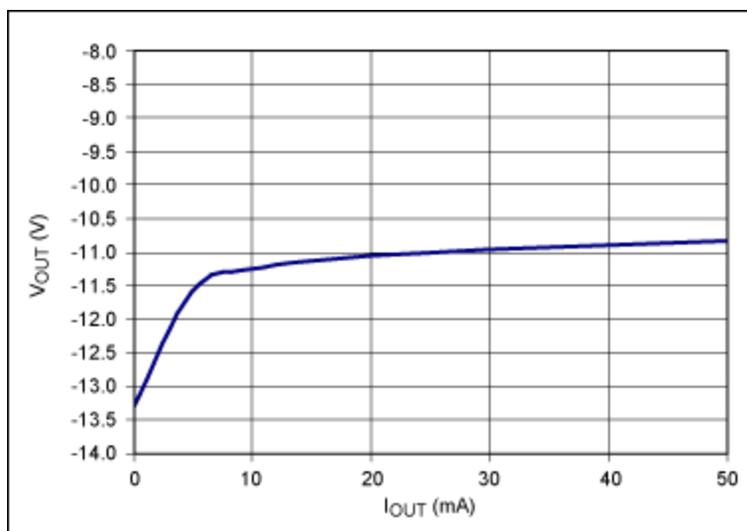


Figure 2. Negative supply load regulation. With a 50mA load connected to the +12V output in Figure 1, this graph shows typical load regulation of the -12V output.

The MAX1896's constant-frequency operation allows simple filtering and produces less noise than a frequency-modulation scheme. The high switching frequency is easily filtered with passive LC filters or with external transistor-buffered RC filters, as shown in Figure 1. As always for switching converters, a good PC-board layout is essential for low-noise operation. Further advice on these matters is available in the MAX1896 data sheet.

#### Related Parts

[MAX1896](#)

1.4MHz SOT23 Current-Mode Step-Up DC-DC Converter

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 4434: <http://www.maximintegrated.com/an4434>

APPLICATION NOTE 4434, AN4434, AN 4434, APP4434, Appnote4434, Appnote 4434

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>