



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Amplifiers](#) > APP 5718

Keywords: single device, pulse-width modulation (PWM), waveform generator

APPLICATION NOTE 5718

# Simple Solutions for a Single-Device Pulse-Width Modulation (PWM) Waveform Generator

By: Budge Ing  
Oct 25, 2013

*Abstract: Pulse-width modulation (PWM) generators are integrated in nearly every switching power device. The methods of implementing integrated PWM generators are well-known. This application note is prompted by a customer who asked for a single-device standalone analog PWM waveform generator.*

A similar version of this article appears on [EDN](#), September 25, 2013.

Pulse-width modulation (PWM) generators are integrated in nearly every switching power device. This article shows two methods for implementing a stand-alone analog PWM waveform generator. These designs can also be modified to make a dual-device PWM generator.

There are two ways to implement a single-device PWM waveform generator. One method uses an [ICM7555](#) timer, while the other uses a [MAX998](#) low-power comparator. We will look at each.

## Method 1: Use a Low-Power Timer as a PWM Generator

In this method an ICM7555 timer is configured as in [Figure 1](#).

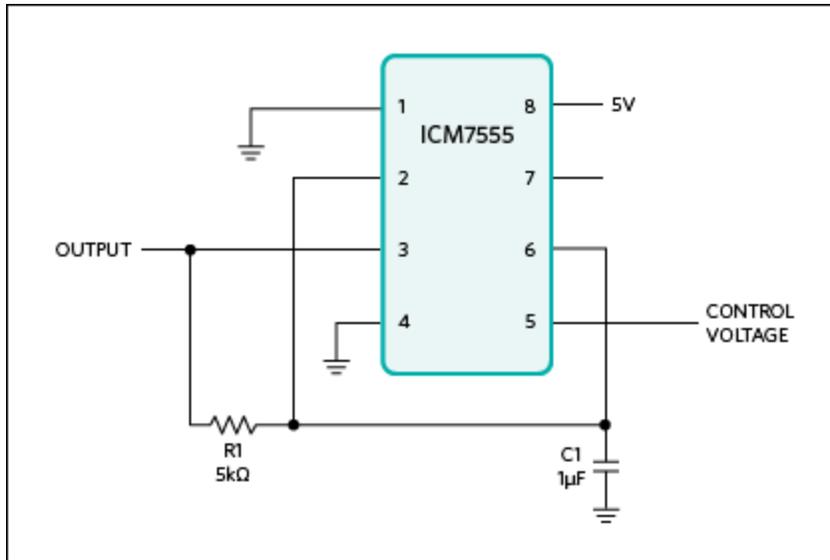


Figure 1. A PWM generator and timer for a single device.

In Figure 1 the pulse width of the output at Pin 3 is modulated by the control voltage ( $V_{\text{CONTROL}}$ ) applied at Pin 5. Lab tests were done on the design with the power supply set at 5V. **Figures 2** through **5** show the PWM output at three different control voltages, 1V, 2V, and 4V. C1 is charged to  $V_{\text{CONTROL}}$  by the supply voltage ( $V_{\text{SUPPLY}}$ ) and discharged from  $V_{\text{CONTROL}}/2$  to ground. When no external control voltage is applied,  $V_{\text{CONTROL}}$  is at  $2/3$  of  $V_{\text{SUPPLY}}$ .

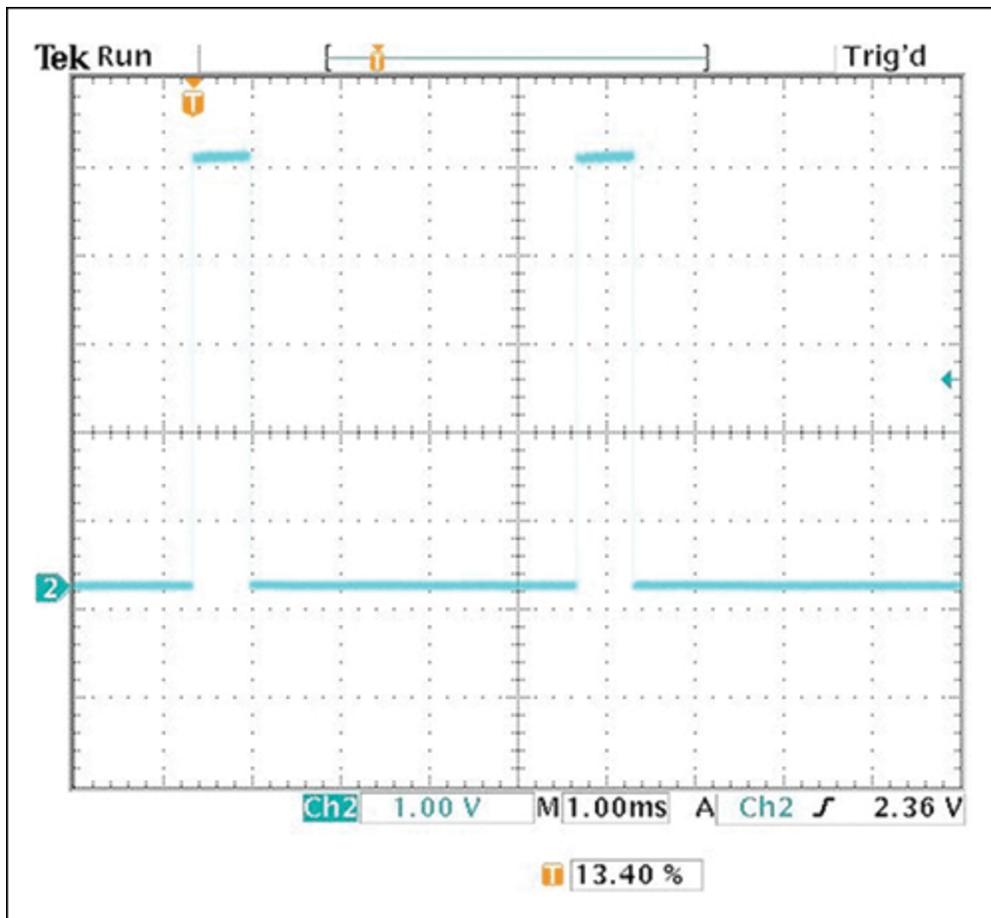


Figure 2. PWM output with control voltage = 1V.

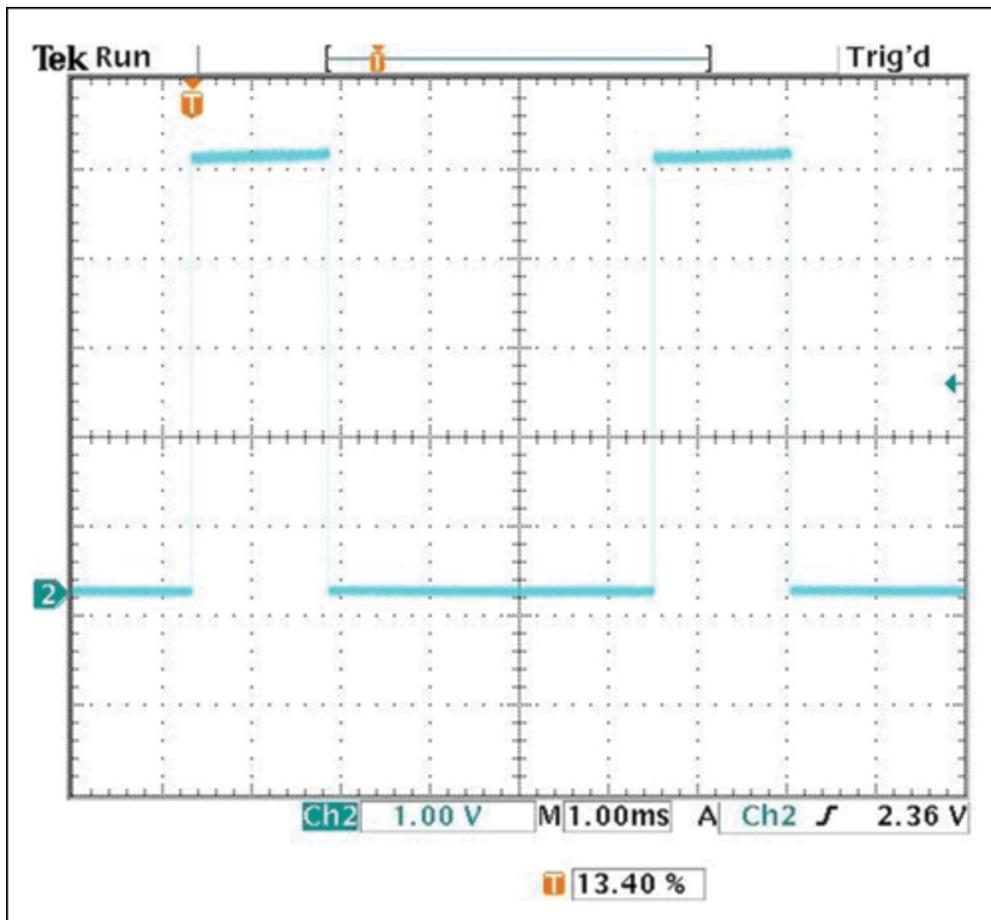


Figure 3. PWM output with control voltage = 2V.

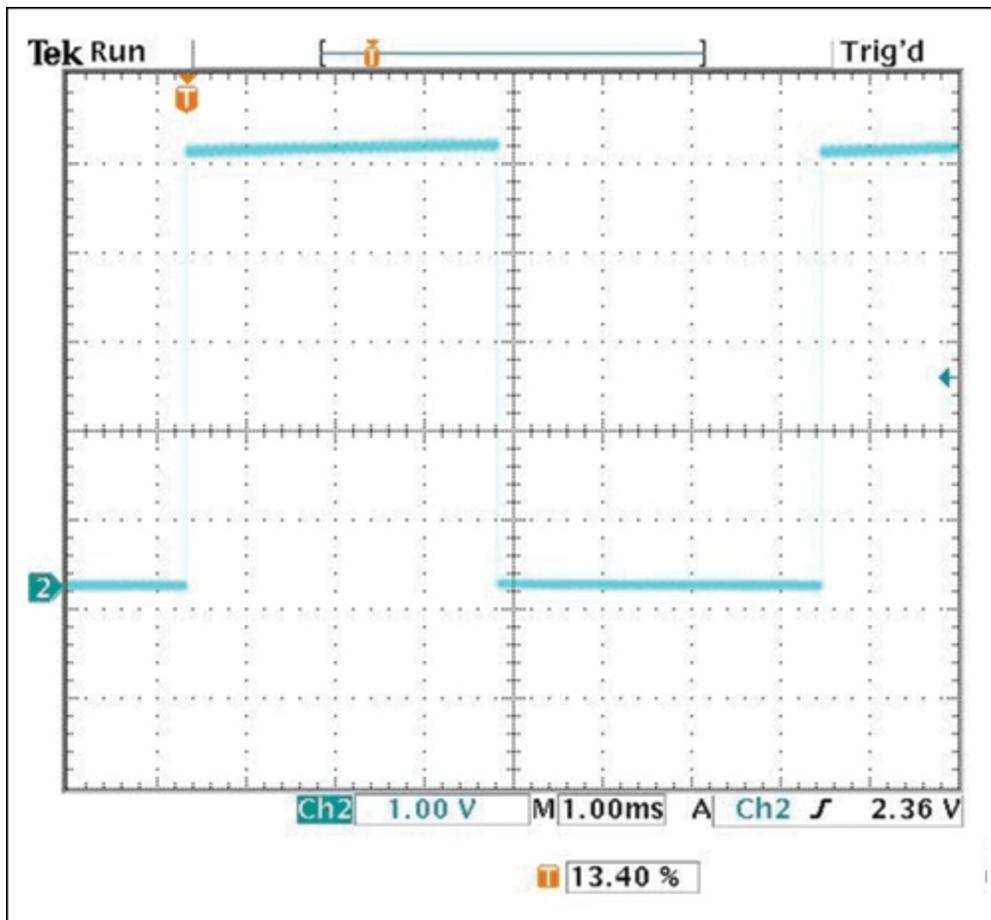


Figure 4. PWM output with no control voltage.

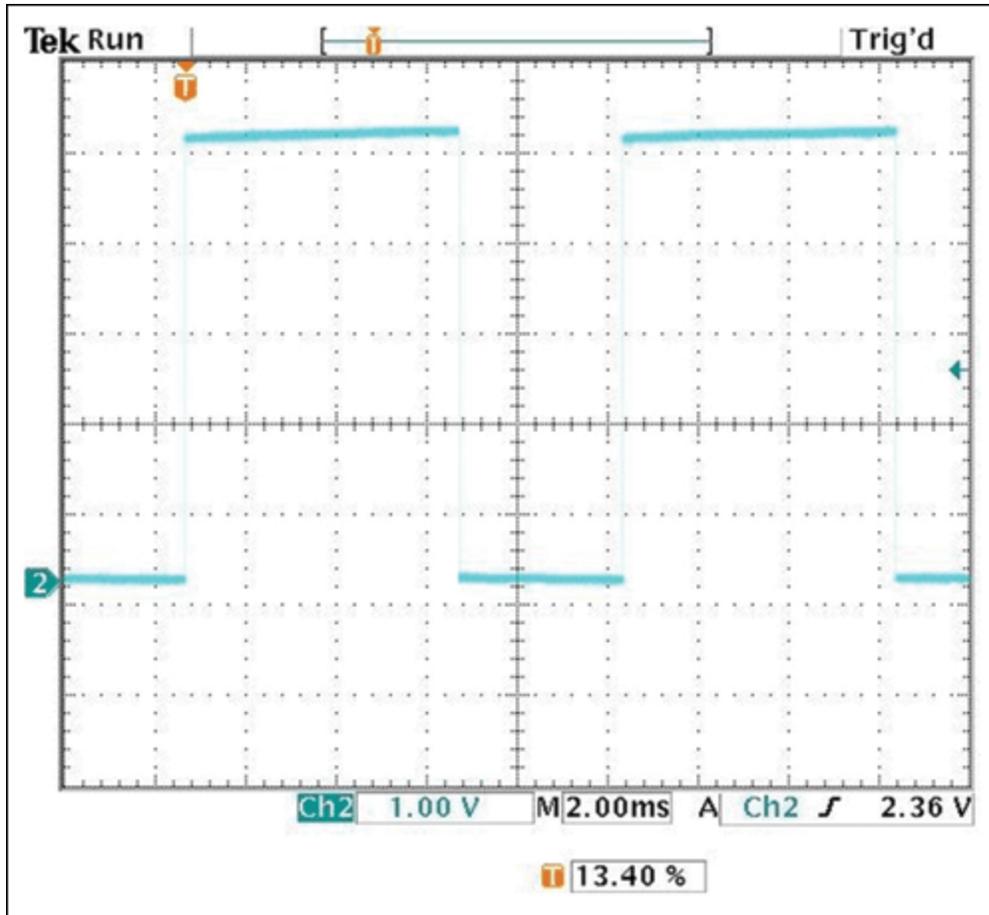


Figure 5. PWM output with control voltage = 4V.

The data illustrate how the control voltage applied at Pin 5 changes the threshold voltage of the two internal comparators. Without the applied control voltage (Figure 4), the device sets the charging and discharging of C1 at 1/3 and 2/3 of the supply voltage. This is equidistant from the supply voltage and ground, thus effecting a 50% duty cycle. The different control voltages change the charging time for C1 to reach  $V_{CONTROL}$  and the discharging time for C1 to discharge to  $V_{CONTROL}/2$ . This process alters the pulse width of the output waveform.

The charging time is expressed as:

$$-t/RC = \ln [1 - (V_{CONTROL}/(2V_{SUPPLY} - V_{CONTROL}))]$$


The discharging time is expressed as:

$$-t/RC = \ln 0.5$$

where  $R = R1$  and  $C = C1$ .

## Method 2: A PWM Generator with Comparator

In this method a MAX998 comparator is configured as in **Figure 6**.

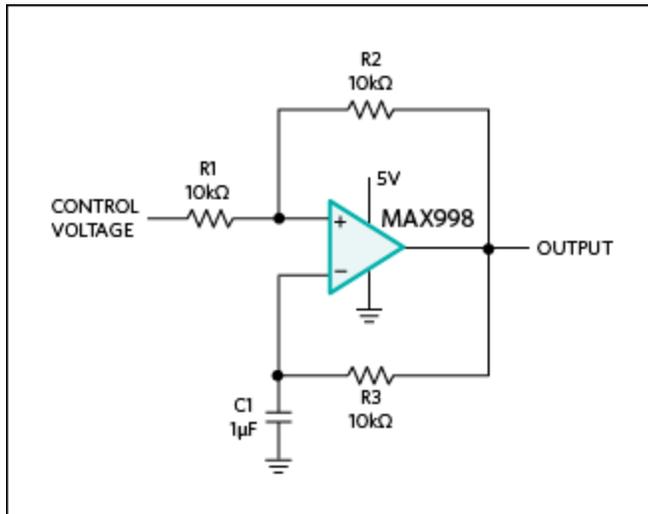

*Figure 6. A PWM generator and comparator.*

The pulse width of the output is modulated by the control voltage applied at R1. Lab tests were done with the power supply set at 5V. **Figures 7** through **9** show the PWM output of three different control voltages, 1V, 2V, and 3V.

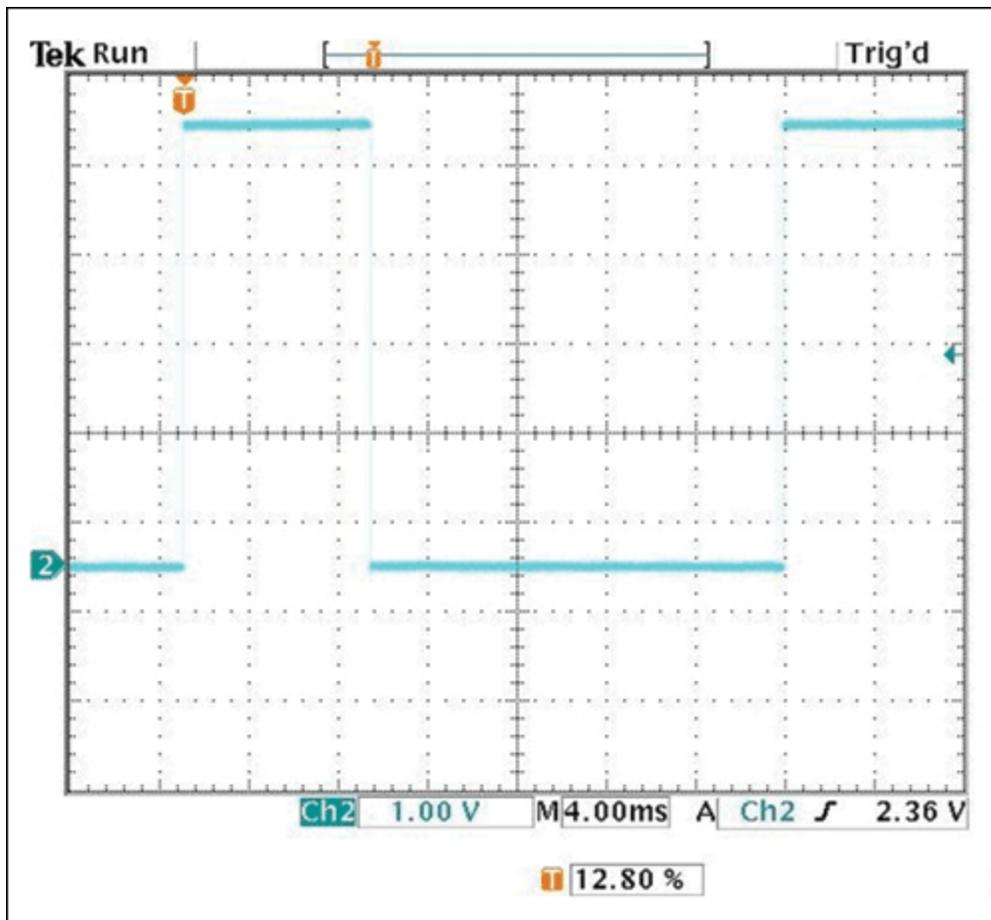


Figure 7. PWM output with control voltage = 1V.

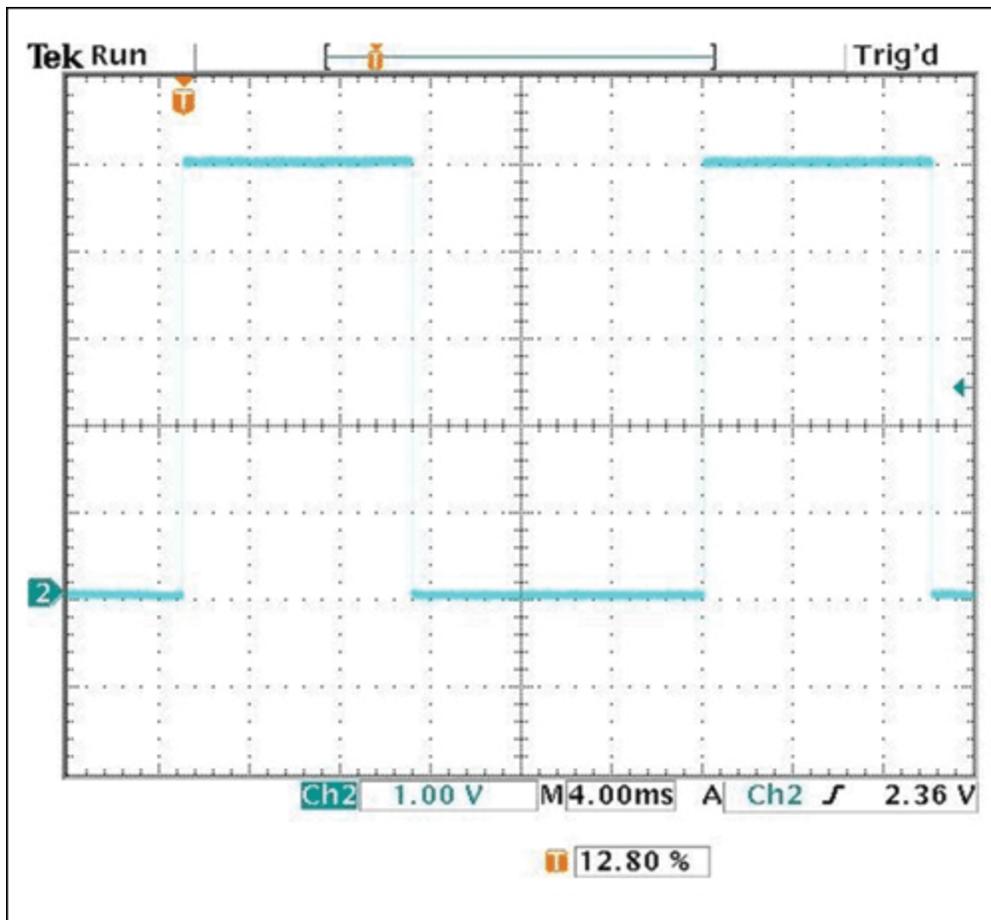


Figure 8. PWM output with control voltage = 2V.

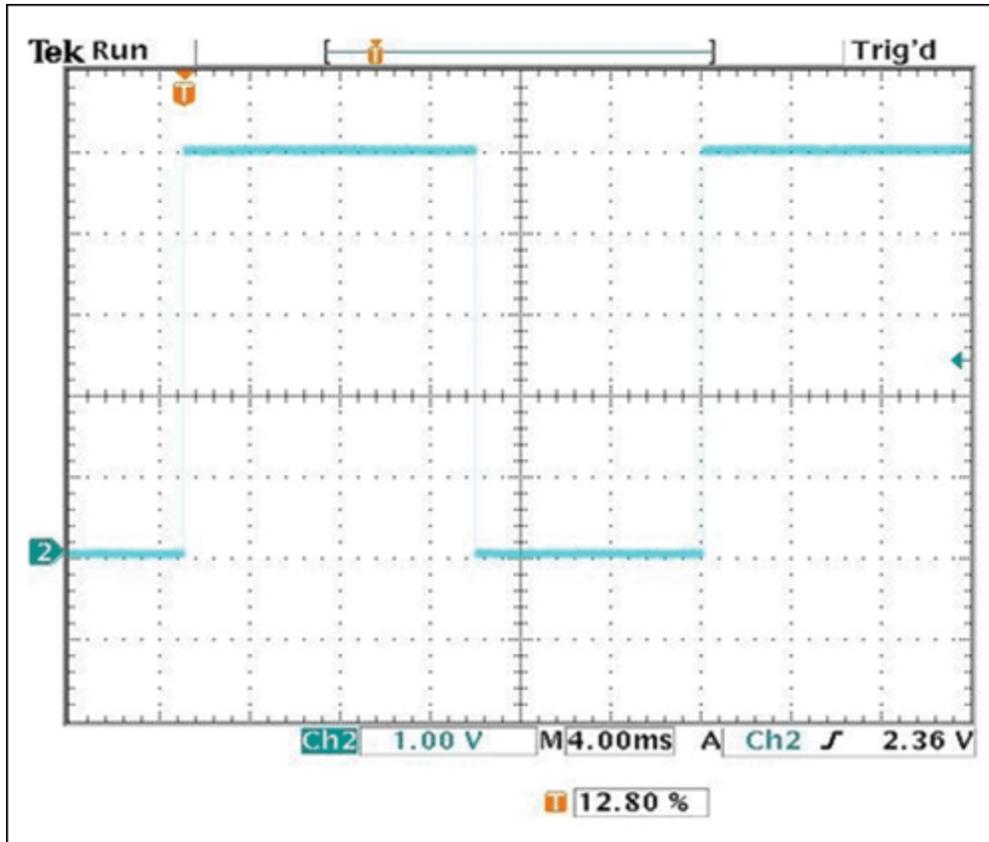


Figure 9. PWM output with control voltage = 3V.

The control voltage applied to the MAX998 sets the threshold voltages at which charging and discharging occur. The upper threshold voltage is  $(V_{\text{SUPPLY}} - V_{\text{CONTROL}})/2 + V_{\text{CONTROL}}$  and the lower threshold voltage is  $V_{\text{CONTROL}}/2$ .

The charging time is expressed as:

$$-t/RC = \ln [1 - (V_{\text{SUPPLY}}/(2 \times V_{\text{SUPPLY}}) - V_{\text{CONTROL}})]$$

The discharging time is expressed as:

$$-t/RC = \ln [1 - (V_{\text{CONTROL}}/(V_{\text{SUPPLY}} + V_{\text{CONTROL}}))]$$

where  $R = R1$  and  $C = C1$ .

### Modifications for a Dual-Device PWM Generator

It is important to note that the control voltage also changes the frequency in both circuit methods. Thus, an additional comparator to the circuits of Method 1 and Method 2 transforms each into a fixed-frequency, dual-device PWM generator.

For Method 1, feed the sawtooth signal at Pin 6 into an input of the second comparator. A voltage

applied at the second comparator's input sets the duty cycle of the fixed-frequency output. Similarly for Method 2, feed the sawtooth signal at the MAX998's negative input into the input of the second comparator. A voltage applied at the second comparator's input sets the duty cycle of the fixed-frequency output.

#### Related Parts

<a href="#">ICM7555</a>	Low-Power, General-Purpose Timer	<a href="#">Free Samples</a>
<a href="#">MAX998</a>	Single/Dual/Quad, SOT23, Single-Supply, High-Speed, Low-Power Comparators	<a href="#">Free Samples</a>

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 5718: <http://www.maximintegrated.com/an5718>

APPLICATION NOTE 5718, AN5718, AN 5718, APP5718, Appnote5718, Appnote 5718

© 2013 Maxim Integrated Products, Inc.

Additional Legal Notices: <http://www.maximintegrated.com/legal>