



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Battery Management](#) > APP 657
[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Power-Supply Circuits](#) > APP 657

Keywords: load disconnect, step-up regulator, boost converter, NiMH output, regulator feedback step-up DC-DC converter

APPLICATION NOTE 657

Simple Circuit Disconnects Load

Jun 19, 2000

Abstract: This application note shows how an external power MOSFET acts as a load-disconnect switch and allows a switching regulator to start up with heavy loads and low-input voltages. The load-disconnect circuit boosts a single NiMH cell output to 3.3V and delivers output currents to 600mA. The MAX1703 step-up DC-DC converter is featured in the design.

Placing a load-disconnect circuit on the output of a bootstrapped step-up regulator allows the regulator to start with load currents much higher than would otherwise be possible (**Figure 1**). During shutdown, the disconnect completely isolates the battery from the load. The circuit boosts a single NiMH-cell output to 3.3V and delivers output currents to 600mA. Step-up regulators are excellent for portable applications because they exhibit high efficiency, low supply current (120 μ A operating, 20 μ A in shutdown), and ample current once started. Many, however, cannot start with maximum load from low supply voltages, such as those from single-cell batteries. This problem arises because most low-voltage CMOS boost regulators derive power from their own outputs, which equal V_{IN} minus a diode drop at start-up. Low values of input voltage don't allow the switching transistor to become fully enhanced at start-up, so the transistor presents a high impedance that limits the peak inductor current. As a result, the circuit cannot produce enough current to simultaneously supply the load and charge the output capacitor.

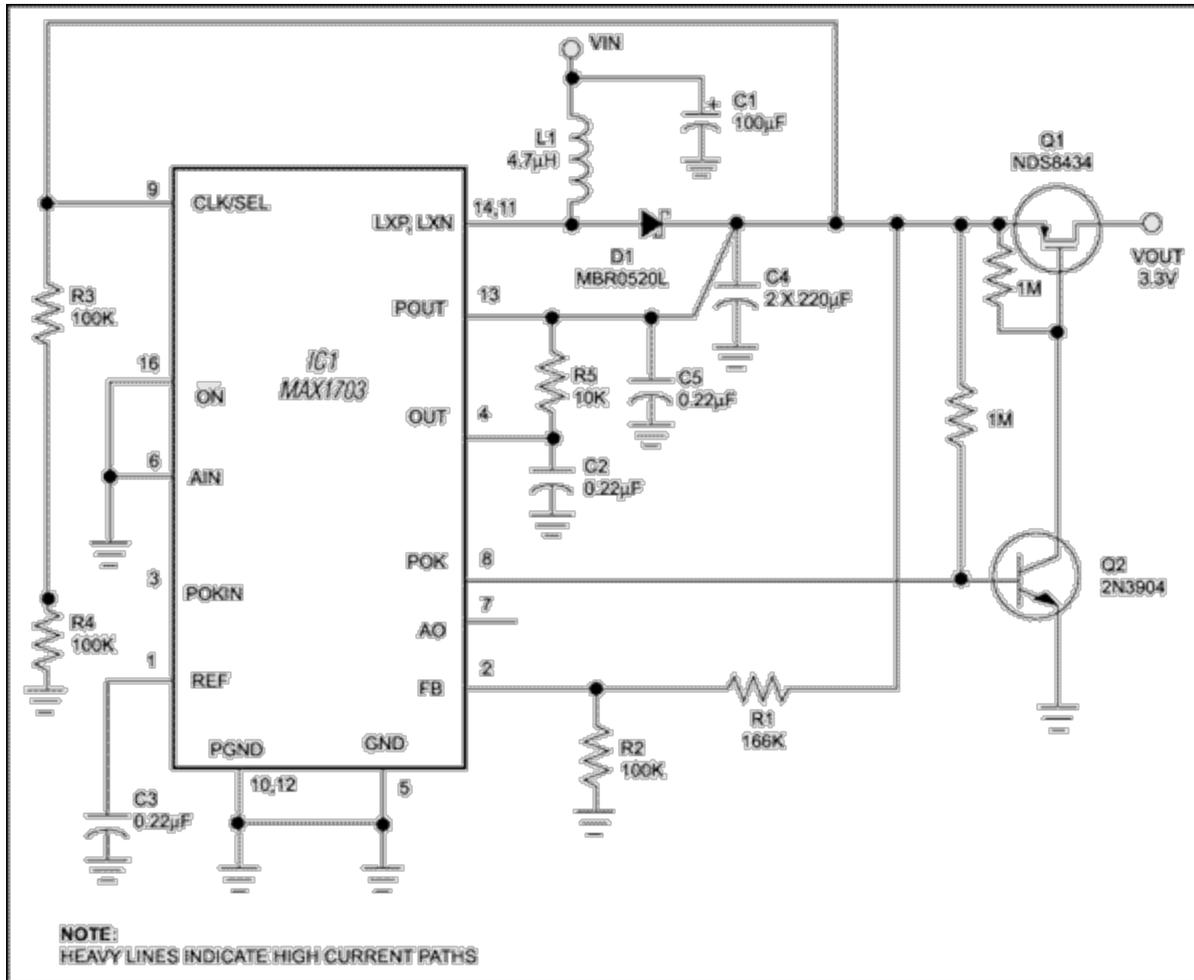


Figure 1. The addition of a couple of transistors enables a switching regulator to start with full load and low input voltages.

To get around this problem and ensure reliable start-ups, most regulator ICs incorporate an undervoltage lockout (UVLO). IC₁, for example, is a synchronous boost converter whose bootstrapped operation cannot start until its output voltage exceeds the internal UVLO threshold of 2.3V. You can overcome this start-up limitation with an external power MOSFET, Q₁, operating as a load-disconnect switch, and by using the power-OK (POK) comparator built into many low-voltage switching regulators. R₃ and R₄ set the POK threshold at 2.5V, allowing V_{IN} to rise above the UVLO threshold. Q₂ inverts the POK output before driving Q₁. Q₁ disconnects the load, allowing V_{OUT} to rise to a level (above UVLO) that ensures full enhancement of Q₁ when it turns on. As a result, the circuit can start under full load with input voltages as low as 0.8V (**Figure 2a**). Because the circuit takes the regulator feedback before this switch, the MOSFET you choose for a given application depends on the load current and minimum acceptable level of load regulation. The MOSFET shown is a low-threshold device. Connecting the FB terminal (Pin 2) to ground and removing R₁ and R₂ produces a 5V regulated output, whose performance is similar to that of the 3.3V version (**Figure 2b**). (DI #2487)

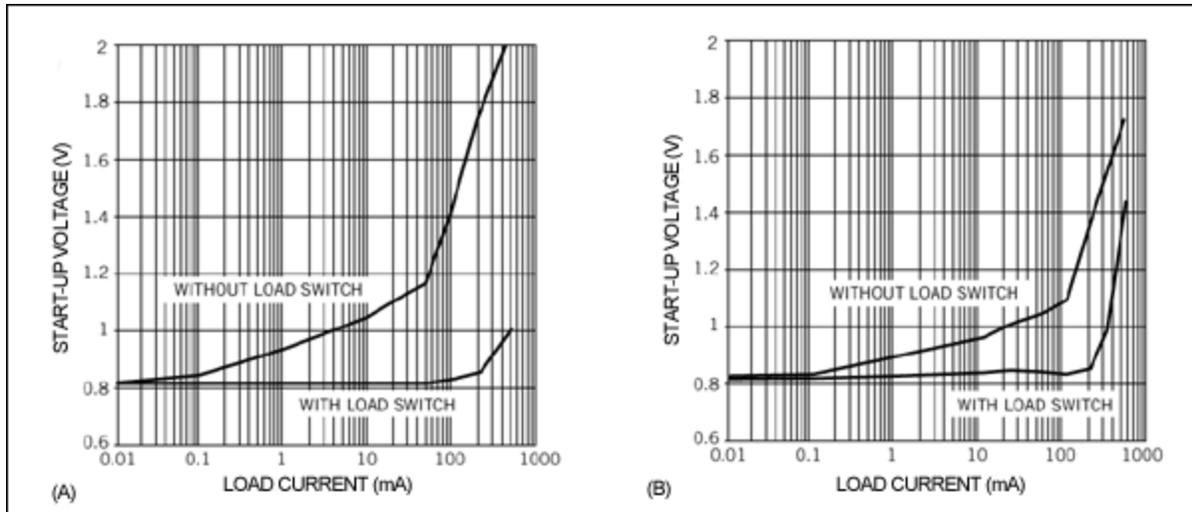


Figure 2. The load-disconnect switch in Figure 1 allows the regulator to start up with heavy loads and low input voltages (a). A slight modification of the circuit in Figure 1 provides 5V-output operation (b).

Reprinted from EDN magazine February 17, 2000
 Copyright Cahners Business Information 2000
 A Division of Reed Elsevier Inc.

Related Parts

MAX1703

1-Cell to 3-Cell, High Power (1.5A), Low-Noise, Step-Up DC-DC Converter

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 657: <http://www.maximintegrated.com/an657>

APPLICATION NOTE 657, AN657, AN 657, APP657, Appnote657, Appnote 657

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>