



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Automotive](#) > APP 725

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Power-Supply Circuits](#) > APP 725

Keywords: power supply, voltage converter, dc-dc converters, charge pumps, switched capacitor regulator, regulated charge pump, unregulated charge pump, voltage divider, voltage doubler, regulated inverter, buck-boost, regulator, charge pump power dissipation

TUTORIAL 725

DC-DC Conversion Without Inductors

Jul 22, 2009

Abstract: Charge pumps are often the best choice for powering an application that requires both low power and low cost. This application note discusses integrated charge pumps and explains how to calculate power dissipation in a charge pump.

A familiar problem in system engineering is the subsystem whose power requirements are not met by the main supply. In such cases, the available supply rails are not directly usable, nor is the direct use of battery voltage (when available) always an option. Lack of space can prevent inclusion of the optimal number of cells, or the declining voltage of a discharging battery may not be acceptable for the application.

Voltage converters can generate the desired voltage levels, and charge pumps are often the best choice for applications requiring some combination of low power, simplicity, and low cost. Charge pumps are easy to use, because they require no expensive inductors or additional semiconductors.

Charge Pumps—A General Description

Charge-pump voltage converters use ceramic or electrolytic capacitors to store and transfer energy. Although capacitors are more common and much cheaper than the coils used in other types of DC-DC converters, capacitors cannot change their voltage level abruptly. A changing capacitor voltage always follows the exponential function, which imposes limitations that inductive voltage converters can avoid. Inductive voltage converters are, however, more expensive.

Capacitive voltage conversion is achieved by switching a capacitor periodically. Passive diodes can perform this switching function in the simplest cases, if an alternating voltage is available. Otherwise, DC voltage levels require the use of active switches, which first charge the capacitor by connecting it across a voltage source and then connect it to the output in a way that produces a different voltage level.

A common integrated circuit using this principle is the [ICL7660](#), which some consider the prototype of the classic charge pump. The ICL7660 integrates switches and the oscillator so that the switches S1, S3 and S2, S4 work alternately (**Figure 1**). The configuration shown here inverts the input voltage. With a slight change in the external connections, it can double or divide the input voltage as well.

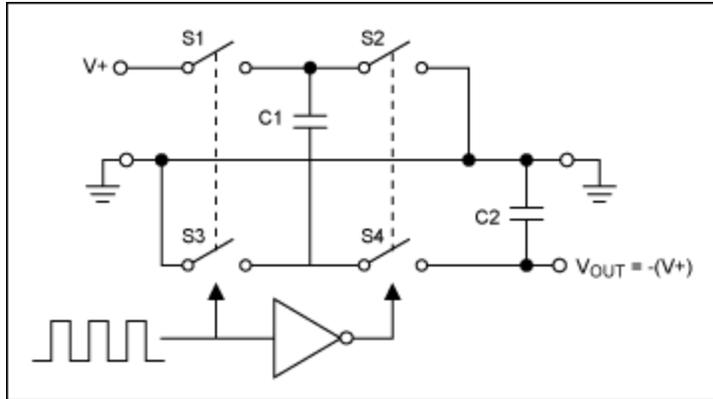


Figure 1. These essential components illustrate the mechanics of charge-pump operation.

Closing S1 and S3 charges the flying capacitor, C1, to $V+$ in the first half cycle. In the second half, S1 and S3 open and S2 and S4 close. This action connects the positive terminal of C1 to ground and connects the negative terminal to V_{OUT} . C1 is then in parallel with the reservoir capacitor C2. If the voltage across C2 is smaller than that across C1, charge flows from C1 to C2 until the voltage across C2 reaches $-(V+)$.

An integrated fixed-frequency oscillator drives the periodic switching. This circuit has no output regulation, and the switching frequency remains constant for all loads. Thus, the output-voltage variation depends strongly on the load. With no load, the output voltage corresponds to the negative input voltage: $V_{OUT} = -(V+)$. As the load increases, V_{OUT} decreases. Output current for the ICL7660 is, therefore, limited to about 10mA. This is partly due to its low oscillator frequency, and partly due to its integrated analog switches which are far from ideal. These switches in the "on" state exhibit several ohms of on-resistance. A detailed calculation of the resulting power dissipation will be shown later.

Pin-compatible circuits ([MAX660](#), [MAX860/MAX861](#), [MAX1680/MAX1681](#)) feature higher switching frequencies and lower on-resistance in the switches. Because their switching frequencies are higher, these charge pumps operate with smaller capacitors and deliver higher output current. All the devices can be configured as a voltage inverter, doubler, or divider.

The [MAX828/MAX829](#) and [MAX870/MAX871](#), which were designed for inverter applications, reduce the required board area with a smaller package (SOT23) and smaller external capacitors. Pin-compatible versions of these devices ([MAX1719/MAX1720/MAX1721](#)) provide an additional shutdown pin for switching off the circuit. In that condition, the supply current drops to 1nA, the output disconnects from the input, and the output voltage drops to zero.

Capacitive Voltage-Divider

Consider a circuit designed to divide the input voltage by two and double the output current. It offers advantages over linear regulators (which usually convert power into heat), and benefits applications that require a limited output current. A 4mA to 20mA interface, for example, often provides a relatively high output voltage but a limited preset output current. Other applications include the many op amps and microcontrollers that now operate with very low supply voltages. In those circuits, dividing the supply voltage by two theoretically divides the power consumption by four.

The configuration of **Figure 2** generates a regulated $V_{OUT} (= V_{IN}/2)$ using the capacitive voltage divider C3, C4 and C5, C6. By switching the flying capacitor, C2, alternately between upper and lower halves of this divider, the IC counterbalances any load-dependant voltage differences. The circuit's switching

frequency is 35kHz and its quiescent current is only 36 μ A. When load currents exceed 1mA, the circuit's efficiency exceeds 90%. Given very small load currents (i.e., below 100 μ A), however, even this low 36mA quiescent current reduces conversion efficiency. This switched-capacitor configuration provides both better regulation than a simple resistive voltage-divider, and higher efficiency than that obtained from a simple combination of a voltage-divider and an op-amp buffer. The IC specification limits V_{IN} to 5.5V maximum.

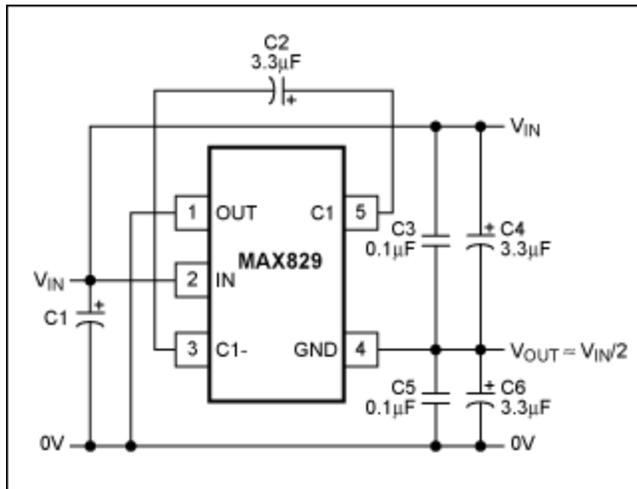


Figure 2. With the connections shown, this inverting charge-pump IC divides the input voltage by two.

Calculating Charge-Pump Power Dissipation

Consider now a simple model in which a capacitor, C1, switches between the output voltage and V_+ at frequency f (Figure 3). This model enables a discussion of charge-pump power dissipation.

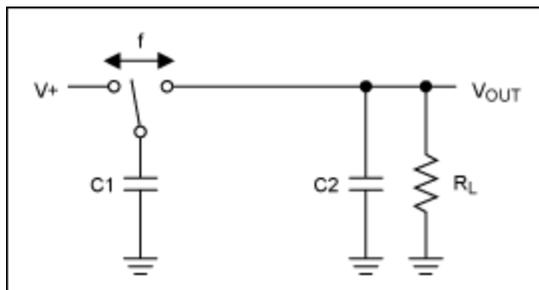


Figure 3. This model of a switched capacitor shows that it behaves like a resistor.

A reservoir capacitor, C2, and load, R_L , are connected to V_{OUT} . The charge transmitted per cycle is:

$$\Delta Q = C1(V_+ - V_{OUT})$$

Which produces a current, I , that depends on the frequency f :

$$I = f\Delta Q = fC1(V_+ - V_{OUT}).$$

After changing the equation according to Ohm's Law, an equivalent resistance, R_{ERS} , for the switched capacitor can be calculated as:

$$R_{ERS} = 1/fC1$$

This equation shows that the resistance and, consequently, the resistive losses decrease with increasing frequency and higher capacitance. Higher capacitance lowers the output resistance only until the switches' resistance and the capacitors' equivalent series resistance (ESR) exceed R_{ERS} . This internal loss (switching loss) can be reduced only by choosing low-ESR capacitors. Switch on-resistance can be lowered through the use of sophisticated new charge pumps.

Switching loss is caused by the voltage difference between the flying capacitor and the output capacitor, as well as by on-resistance in the switches. This voltage difference appears across the switches, causing dissipation in the application. As shown before, a switched capacitor behaves like a resistance. Thus, you can reduce output resistance and increase the output power by connecting several switched-capacitor devices in parallel.

Regulated Charge Pumps

Integrated charge pumps that regulate the output voltage operate without inductors. They offer regulated output voltages (e.g., 5V) and several power-saving modes. Devices such as the [MAX682](#) regulated upconverters operate either in the efficient skip mode or in a fixed-frequency mode with reduced output ripple.

When a drop in output voltage is sensed by the internal comparator, the power-saving skip mode avoids unnecessary switching by activating only the internal oscillator. The result is lower quiescent current and lower switching dissipation, especially for light loads. Skip mode is preferable for low-power applications, because higher levels of quiescent current reduce overall efficiency.

To minimize output ripple, the circuit can oscillate in a fixed-frequency mode that is regulated between 50kHz and 2MHz. Regulation ensures that the flying capacitor is charged through an internal MOSFET with a charging current that depends on the load. A decreasing output voltage, caused by increasing power consumption, charges the capacitor with more energy. As benefits of the fixed-frequency mode, the output ripple is lower and the external components are smaller. If you have the impression that charge pumps provide only low output currents of a few milliamps, you will be surprised to learn that the MAX682 delivers as much as 250mA from a 5V output.

Regulated-Charge-Pump Design Idea

An improved design for maintaining a switching frequency that is constant and independent of the input voltage is shown in **Figure 4**.

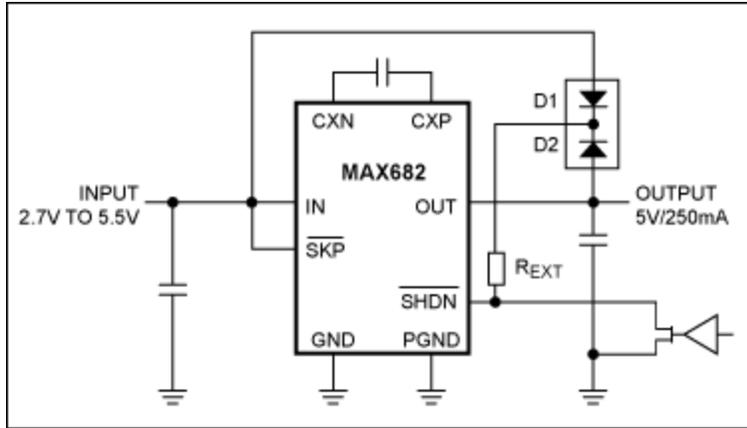


Figure 4. This regulated charge pump maintains a constant switching frequency.

The IC's internal switching frequency is controlled with current into its shutdown pin. The governing equation is taken from the device's data sheet:

$$R_{EXT} = 45000(V_{IN} - 0.69V)/f_{OSC}, \text{ with } R_{EXT} \text{ in } k\Omega \text{ and } f_{OSC} \text{ in } kHz$$

Normally, you calculate the value of the external shutdown resistor with the given input voltage and the desired switching frequency. In this case, however, the equation shows that switching frequency and current in the shutdown pin depend on the input voltage, V_{IN} . If the input voltage varies, the switching frequency varies too.

Two diodes direct current into the shutdown pin. D1 ensures a reliable startup by directing current from the input to the shutdown pin when the supply voltage is first turned on. When the output voltage achieves 5V or rises higher than V_{IN} , the switching frequency becomes constant because D2 conducts current from the stable output voltage. A tiny diode array in a 3-pin SOT23 package (BAV70) is recommended for the D1-D2 combination. Note that a shutdown function is still available. Driving the shutdown pin to ground with an open-drain MOSFET simply short circuits the preset-frequency current to ground.

Regulated Inverter

Many applications need an additional negative voltage such as -5V. Such a voltage can be generated with a regulating charge-pump inverter ([MAX868](#)) and a few external components (**Figure 5**). When charging, the left-side switches close and the right-side switches open. Both flying capacitors are charged in parallel, and the load is serviced entirely by charge stored in the output capacitor. During discharge, the switches reconfigure to connect the flying capacitors in series. When connected to the output capacitor, they then transfer charge as required to maintain output-voltage regulation.

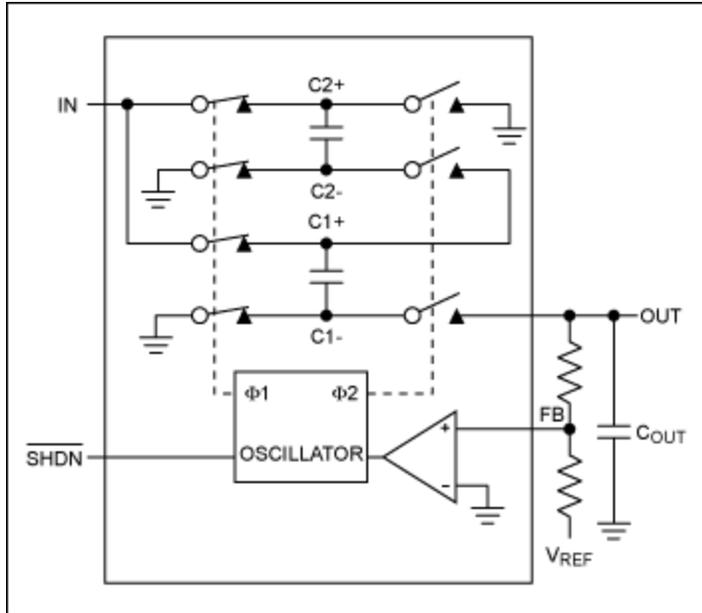


Figure 5. Internal components illustrate the operation of this regulated charge-pump inverter (MAX868).

The internal oscillator frequency (450kHz) is sufficiently high to ensure small external capacitors and high output current. Controlled by a comparator, the oscillator becomes active only when the output voltage is lower than its threshold. This regulation enables the circuit to provide constant output voltages as high as $-2V_{IN}$. At the same time, the circuit draws minimum quiescent currents at light loads.

Buck/Boost Combination

Another problem common in battery-powered applications is a battery voltage that ranges above and below the regulated output voltage. The output voltage of a Li+ cell varies from 3.6V to 1.5V during its lifetime, before it is recharged. To derive a constant 3.3V from this changing input, a combined buck/boost converter is required. Initially this device downconverts the full battery voltage (3.6V) to 3.3V. When the battery voltage drops below 3.3V, the step-up converter function guarantees the regulated 3.3V output voltage.

Though usually complicated, this approach can now be implemented with a simple charge-pump IC like the [MAX1759](#). Operating from input voltages ranging from 1.6V to 5.5V, the MAX1759 generates an output either fixed (3.3V) or adjustable (2.5V to 5.5V) and delivers output currents up to 100mA. This IC comes in a 10-pin μ MAX[®] package and operates with three external capacitors. An additional shutdown mode disconnects output from input while lowering the quiescent current to 1 μ A.

Charge-Pump Overview

Tables 1 and **2** list some of the regulated and unregulated charge pumps available from Maxim, including those with special functions and all those mentioned in the text. These tables enable designers to choose a suitable charge pump according to the application's required package, functions, and output-current specifications.

Maxim continually introduces new products. We encourage you to browse Maxim's product lines for the most updated list of charge-pump devices. Capacitor charge pumps are shown under the [Power and Battery Management](#) category.

Table 1. Unregulated Charge Pumps

Part Number	Input Voltage	Output Voltage	Output Current	Switching Frequency	Features
MAX828/MAX829	1.5V to 5.5V	$-V_{IN}$	25mA	12kHz/35kHz	Inverter; 5-pin SOT23 package
MAX1720	1.5V to 5.5V	$-V_{IN}$	25mA	12kHz	Inverter; low quiescent current, shutdown, 6-pin SOT23 package
MAX1719/1721	1.5V to 5.5V	$-V_{IN}$	25mA	125kHz	Inverter; 6-pin SOT23 package, shutdown
MAX870/871	1.4V to 5.5V	$-V_{IN}$	25mA	125kHz/500kHz	Inverter; 5-pin SOT23 package
MAX1682/1683	2V to 5.5V	$2 \times V_{IN}$	30mA	12kHz/35kHz	Doubler; 5-pin SOT23 package
ICL7660 MAX1044	1.5V to 10V	$-V_{IN}$, $2 \times V_{IN}$	10mA	10kHz	Doubler or inverter; DIP, 8-pin SO
MAX860	1.5V to 5.5V	$-V_{IN}$, $2 \times V_{IN}$	50mA	6kHz; 50kHz; 130kHz	Doubler or inverter; 8-pin SO/ μ MAX
MAX861	1.5V to 5.5V	$-V_{IN}$, $2 \times V_{IN}$	50mA	13kHz; 100kHz; 250kHz	Doubler or inverter; 8-pin SO/ μ MAX
MAX1680	2V to 5.5V	$-V_{IN}$, $2 \times V_{IN}$	125mA	125kHz; 250kHz	Doubler or inverter; 8-pin SO/ μ MAX
MAX1681	3V to 5.5V	$-V_{IN}$, $2 \times V_{IN}$	125mA	500kHz; 1MHz	Doubler or inverter; 8-pin SO/ μ MAX

Table 2. Regulated Charge Pumps

Part Number	Input Voltage	Output Voltage	Output Current	Switching Frequency	Features
MAX619	2V to 3.6V	+5V	50mA	500kHz	Regulated 5V, 8-pin SO package
MAX682	2.7V to 5.5V	+5V	250mA	50kHz to 2MHz	Regulated 5V, 8-pin SO/ μ MAX packages
MAX868	1.8V to 5.5V	Up to $-2 \times V_{IN}$	30mA	up to 450kHz	Variable inverted voltage; μ MAX package
MAX1673	2.0V to 5.5V	Up to $-V_{IN}$	125mA	350kHz	Variable inverted voltage; fixed frequency
MAX1759	1.6V to 5.5V	2.5V to 5.5V	100mA	1.5MHz	Buck/boost converter

μ MAX is a registered trademark of Maxim Integrated Products, Inc.

Related Parts

ICL7660	Switched-Capacitor Voltage Converters	Free Samples
MAX1044	Switched-Capacitor Voltage Converters	Free Samples
MAX1673	Regulated, 125mA Output, Charge Pump DC-DC Inverter	Free Samples
MAX1680	125mA, Frequency-Selectable, Switched-Capacitor Voltage Converters	Free Samples
MAX1681	125mA, Frequency-Selectable, Switched-Capacitor Voltage Converters	Free Samples
MAX1682	Switched-Capacitor Voltage Doublers	Free Samples
MAX1719	SOT23, Switched-Capacitor Voltage Inverters with Shutdown	Free Samples
MAX1720	SOT23, Switched-Capacitor Voltage Inverters with Shutdown	Free Samples
MAX1721	SOT23, Switched-Capacitor Voltage Inverters with Shutdown	Free Samples
MAX1759	Buck/Boost Regulating Charge Pump in μ MAX	Free Samples
MAX619	Regulated 5V Charge Pump DC-DC Converter	Free Samples
MAX682	3.3V Input to Regulated 5V Output Charge Pumps	Free Samples
MAX828	Switched-Capacitor Voltage Inverters	Free Samples
MAX829	Switched-Capacitor Voltage Inverters	Free Samples
MAX860	50mA, Frequency-Selectable, Switched-Capacitor Voltage Converters	Free Samples
MAX861	50mA, Frequency-Selectable, Switched-Capacitor Voltage Converters	Free Samples
MAX868	Regulated, Adjustable -2x Inverting Charge Pump	Free Samples
MAX870	Switched-Capacitor Voltage Inverters	Free Samples
MAX871	Switched-Capacitor Voltage Inverters	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 725: <http://www.maximintegrated.com/an725>

TUTORIAL 725, AN725, AN 725, APP725, Appnote725, Appnote 725

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>