

Keywords: analog switches, THD, audio filter, on-resistance distortion, flatness, linearity impedance

APPLICATION NOTE 730

Minimizing Total Harmonic Distortion Contributed by Analog Switches in Audio Systems

Jan 25, 2002

Abstract: Analog switches are commonly used in audio systems to switch low-level inputs or adjust audio filter characteristics. Selecting the proper analog switch can help optimize the total harmonic distortion (THD) of a system within the designer's cost budget.

Analog switches are commonly used in audio systems to switch low-level inputs or adjust audio filter characteristics. Selecting the proper analog switch can help optimize the total harmonic distortion (THD) of a system within the designer's cost budget.

THD specification plays a critical role in determining the quality or fidelity of audio signals passing through or generated by audio systems. Thus, when designing audio systems, importance must be placed on selecting the proper components and board layout to minimize THD.



Attend this brief webcast by Maxim on TechOnline

When passing a signal through a switch, the switch must not degrade signal integrity or introduce any new information onto the desired output signal. Any change in waveform is considered to be *distortion* and is obviously undesirable and also impossible to avoid, and thus must be minimized.

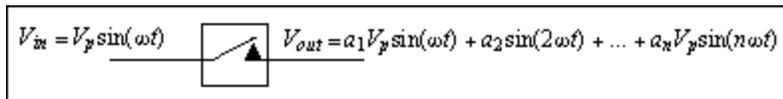


Figure 1.

$$THD = \frac{[a_2^2 + a_3^2 + \dots + a_n^2]^{1/2}}{a_1} \times 100\% \quad (\text{Eq. 01})$$

THD is defined as the square root of the ratio of the sum of all of the squared second, third, and higher harmonics to the magnitude of the fundamental harmonic.

Selecting an analog switch with a minimum THD requires one with low on-resistance (R_{ON}) and consequently low on-resistance flatness ($R_{FLAT(ON)}$). Some analog-switch data sheets neglect to specify flatness, but it can be assumed to be approximately 10% of the on-resistance. Flatness is defined as the

difference between the maximum and minimum values of on-resistance as measured over the specified analog-signal range.

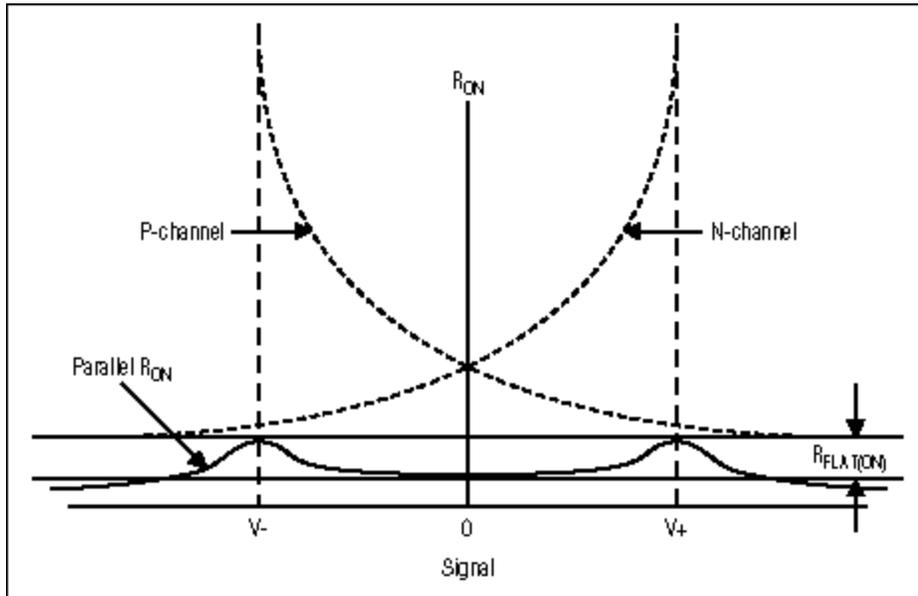


Figure 2. $R_{FLAT(ON)}$.

The on-resistance curves are determined by the length L , width W , electron and hole mobility (μ_n and μ_p , respectively), oxide capacitance C_{OX} , threshold voltage V_T , and signal voltage V_{GS} (V_{IN}) of both MOSFETs.

$$R_{ONn} = \frac{L}{\mu_n C_{OX} W (V_{GS} - V_T)} \quad (\text{Eq. 02})$$

$$R_{ONp} = \frac{L}{\mu_p C_{OX} W (V_{GS} - V_T)} \quad (\text{Eq. 03})$$

As illustrated above, the on-resistance for the PMOS and the NMOS are in parallel, resulting in resistance R , which is a nonlinear function. The source of distortion arises from parallel PMOS and NMOS in series with constant load, causing a nonlinear attenuation of the signal passing through the switch. With multiple switches, THDs will add together. The following schematic shows this resistor-divider relationship of the switch and the load.

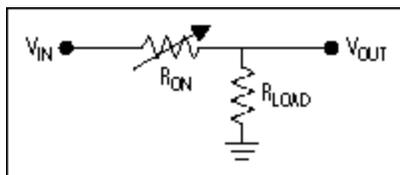


Figure 3.

In practical terms, maximum THD is determined by the following equation:

$$THD_{MAXIMUM} = \frac{R_{FLAT(ON)}}{R_{LOAD}} \times 100\% \approx \frac{10\% \times R_{ON}}{R_{LOAD}} \times 100\% \quad (\text{Eq. 04})$$

As observed in Figure 2, parallel R_{ON} , and therefore $R_{FLAT(ON)}$, can vary depending on the analog input signal, and maximum THD will occur at the greatest difference between the maximum and minimum values of the parallel R_{ON} . Therefore, an analog input signal operating about a point below the maximum value will experience a lower THD.

Three different switches are shown below along with their on-resistance and corresponding measured THD. A standard test load of 10 kilohms was used to obtain the plot.

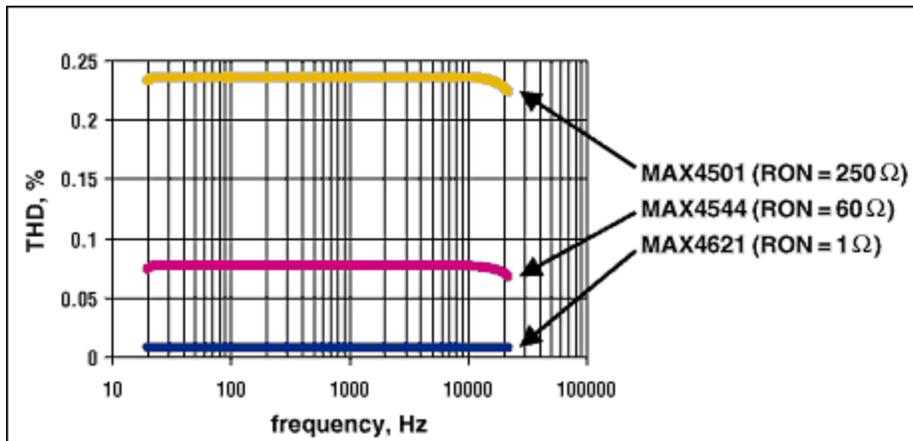


Figure 4. THD vs. frequency.

In audio systems, impedance loads of 1200, 600, 36, 32, 16, 8, 4, and 3 kilohms will be encountered, and, especially with very low impedances, on-resistance flatness ($R_{FLAT(ON)}$) must be taken into consideration to minimize THD. Equation 4 will provide a starting point in selecting an analog switch if THD is the highest priority.

Related Parts

MAX4501	Low-Voltage, SPST, CMOS Analog Switches	Free Samples
MAX4544	Low-Voltage, Single-Supply Dual SPST/SPDT Analog Switches	Free Samples
MAX4621	Dual, 5Ω Analog Switches	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 730: <http://www.maximintegrated.com/an730>

APPLICATION NOTE 730, AN730, AN 730, APP730, Appnote730, Appnote 730

Copyright © by Maxim Integrated Products
Additional Legal Notices: <http://www.maximintegrated.com/legal>