



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Amplifier and Comparator Circuits](#) > APP 741

Keywords: CMVR, CMRR, input voltage range, rail to rail inputs, beyond the rail inputs, op amps, low voltage op amp, low voltage amplifiers

TUTORIAL 741

Rail-to-Rail Outputs and Beyond-the-Rails Inputs: The Inside Story on Micropower Op Amps

Jul 10, 2002

Abstract: When does the input voltage range of a low power/low voltage op amp become important? What operational amplifier should you choose when designing a battery powered handheld system?

To optimize performance in today's low-power handheld systems, designers must pay increasing attention to the common-mode input voltage range, output voltage swing, noise, and supply current of single-supply micropower op amps. Differential op amps usually include the negative rail in their input common-mode range, but that may not be sufficient for applications with extended V_{CM} requirements. For those, Maxim offers its first Beyond-the-Rails op-amp family, whose common-mode input voltage extends not only beyond the negative supply rail but beyond the positive rail as well.

Beyond-the-Rails Inputs

Devices with Beyond-the-Rails inputs are designed especially for low-power single-supply operation. The input stage consists of separate npn and pnp differential-transistor pairs (**Figure 1**). Together, they provide a common-mode input voltage range that extends beyond both supply rails. The npn pair typically connects to the top rail (V_{CC}), and the pnp connects to the bottom rail (V_{EE}).

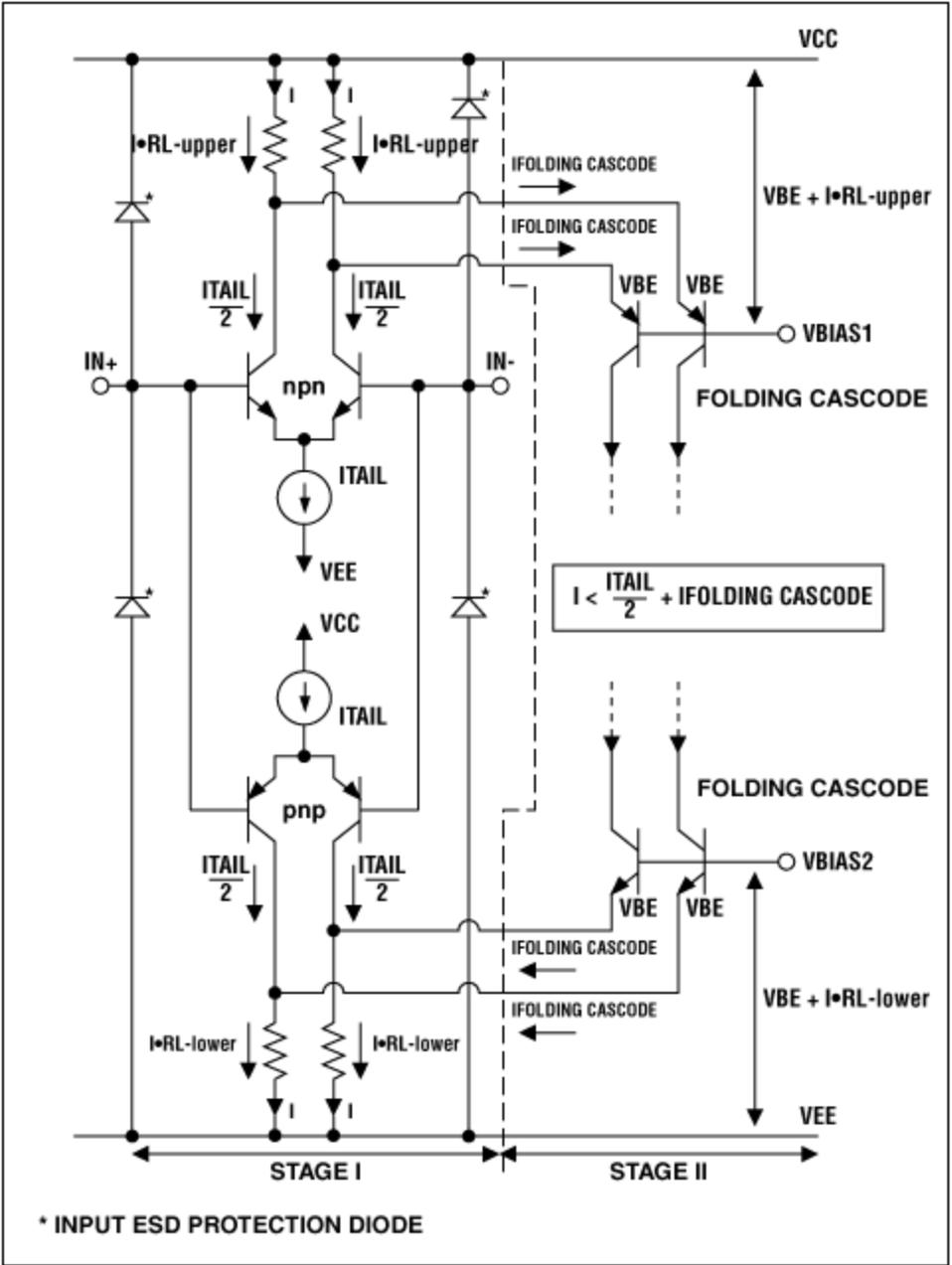


Figure 1. Maxim's Beyond-the-Rails input structure includes overvoltage protection.

To protect sensitive transistor pairs in the input stage, op amps of the MAX4240 family include a 2.2kΩ current-limiting resistor in each input path and separate networks of three back-to-back diodes each for the IN+ and IN- terminals (Figure 2). The forward-voltage drop for these conventional diodes (approximately 0.7V each) results in an overall drop of 2.1V, and the voltage seen by each input (1.45V) is well below the diodes' breakdown level. The resistors limit current in the diode networks to 0.65mA, which is well below the level that could damage the diodes.

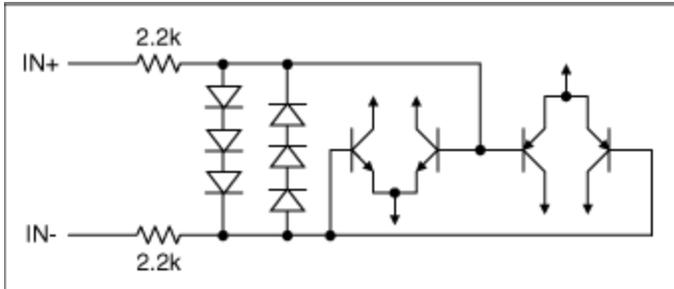


Figure 2. Input protection circuit.

To understand the term "Beyond-the-Rails," you must become familiar with the basic operation of the input structure. For best performance, that is, the highest possible gain (β), transconductance (G_m), and output impedance (Z_{OUT}) the bipolar-transistor pairs used for amplification should operate in their active regions (**Figure 3**). Collector-emitter saturation voltage (V_{CEsat}), the key parameter relating the active and saturated regions, is typically 0.2V or less for transistors in the MAX4240 family of ICs. V_{CEsat} varies slightly with transistor size, collector current, and temperature.

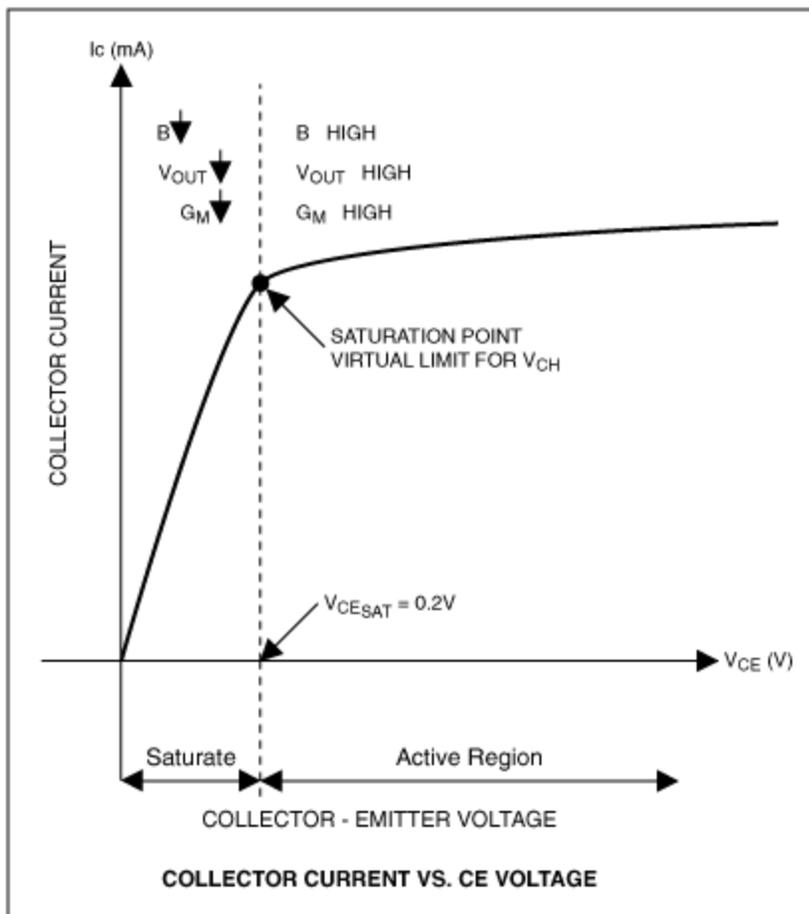


Figure 3. Bipolar signal transistors in the input stage must operate in the active region.

Each input structure contains two npn (or pnp) transistors, two load resistors, and a bias-current source for generating a fixed tail current (I_{TAIL}). For fully balanced transistor pairs that are also ideal, exactly half the tail current flows through each collector path, maintaining a fixed value of voltage across R

upper (or $R_{L\text{-lower}}$). This value is a function of I_{TAIL} and the cascode current ($I_{\text{FOLDING CASCODE}}$) of the second-stage folding-cascode circuit.

The current through load resistors $R_{L\text{-upper}}$ and $R_{L\text{-lower}}$ determines the common-mode input voltage:

$$I = I_{\text{TAIL}}/2 + I_{\text{FOLDING CASCODE}}$$

After choosing a low voltage across the load (0.3V in this case), you set the low end of $R_{L\text{-upper}}$ to $V_{\text{CC}} - 0.3\text{V}$ and the upper end of $R_{L\text{-lower}}$ to $V_{\text{EE}} + 0.3\text{V}$.

Operating the transistor pairs in their active region ensures optimum performance by producing a larger headroom ($> V_{\text{CEsat}}$) between the emitter and the collector. Once the headroom is down to $V_{\text{CE}} = 0.2\text{V}$, however, the transistors begin to saturate, which establishes a limit for the common-mode input range and the acceptable transistor performance ($\beta \downarrow$, $G_m \downarrow$, $Z_{\text{OUT}} \downarrow$). Overshooting the common-mode input range by more than 200mV degrades performance by causing a significant drop in CMRR, but doesn't harm the amplifier. With detailed knowledge of the internal input structure, you can express the upper and lower limits for V_{CM} as follows:

$$V_{\text{CM-upper}} = V_{\text{CC}} - (I * R_{L\text{-upper}} + V_{\text{CEsat(npn)}}) + V_{\text{EB(npn)}}$$

$$V_{\text{CM-upper}} = V_{\text{CC}} - (0.3\text{V} + 0.2\text{V}) + 0.7\text{V}$$

$$V_{\text{CM-upper}} = V_{\text{CC}} + 0.2\text{V}$$

$$V_{\text{CM-lower}} = V_{\text{EE}} + (I * R_{L\text{-lower}} + V_{\text{CEsat(pnp)}}) + V_{\text{BE(pnp)}}$$

$$V_{\text{CM-lower}} = V_{\text{EE}} + (0.3\text{V} + 0.2\text{V}) - 0.7\text{V}$$

$$V_{\text{CM-lower}} = V_{\text{EE}} - 0.2\text{V}$$

When operating on a single +5V supply, the common-mode voltage covers an input range of -0.2V to +5.2V without violating the transistor pairs' saturation condition.

Beyond-the-Rails inputs exhibit a significant change in input bias current as the input signal moves from one supply rail to the other, causing the signal path to shift from one bipolar-transistor pair to the other. This shift between npn and pnp pairs can cause the input bias currents $I_{\text{BIAS+}}$ and $I_{\text{BIAS-}}$ to change polarity and magnitude, producing variations in offset voltage unless the input source impedances seen by IN+ and IN- are equal.

Input resistance is typically 45M Ω for differential input voltages well below 1.8V. Differential inputs greater than 1.8V cause the differential clamp diodes to conduct, producing an input resistance around 4.4k Ω . The amplifier's input bias current can be approximated by the following equation:

$$I_{\text{BIAS}} = (V_{\text{DIFF}} - 1.8\text{V})/4.4\text{k}\Omega$$

As the differential input voltage approaches 1.8V, conduction in the diodes causes the input resistance to decrease exponentially from 45M Ω to 4.4k Ω . Bias current increases with the same exponential curve. To avoid distortion caused by changes in the offset voltage and input bias currents, you can lower the offset error by matching the effective impedances seen at the amplifier's IN+ and IN- inputs.

All MAX4240-MAX4244 amplifier inputs feature diode protection against electrostatic discharge (ESD). The "positive" ESD diode (located between IN+ and V_{CC}) begins conducting when the input voltage exceeds V_{CC} + 0.6V. Similarly, the negative path between IN- and V_{EE} becomes active when IN- overdrives V_{EE} by -0.6V.

Another valuable feature is the inputs' overvoltage protection, which is essential when the operational amplifier is used as a comparator. Without the protective input structure, comparator action drives the positive input high (IN+ to 5V) and the negative input IN- to ground, applying a differential voltage of +5V between the internal pnp and npn pairs. Five volts exceeds the bipolar transistors' maximum allowable reverse emitter-base breakdown voltage (2V). Even if the condition changes instantly, an npn transistor in the IN- path (without protection) would be damaged irreversibly.

Rail-to-Rail Output Stage

Some low-voltage designs don't require Rail-to-Rail or Beyond-the-Rails inputs, but most need Rail-to-Rail output stages to maximize their dynamic performance. The structure of single-supply Rail-to-Rail output stages differs considerably from those in dual-supply operational amplifiers.

Standard output stages typically have an emitter follower structure (**Figure 4a**), but Rail-to-Rail output stages (**Figure 4b**) usually incorporate a common-emitter configuration. The voltage drop in a common-emitter configuration is relatively low and depends only on the emitter-collector saturation voltage V_{CEsat}. Classic emitter-follower output stages, on the other hand, allow the output no closer to the positive rail than V_{CC} - V_{CEsat} - V_{BE}. V_{CEsat} is determined by the internal current source, and V_{BE} is produced by the output transistor.

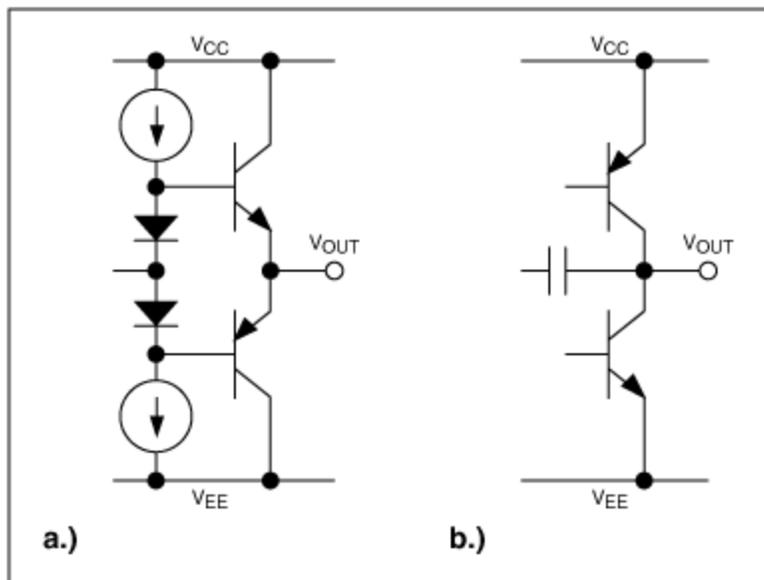


Figure 4. Output stages: the standard emitter-follower configuration (a) and Maxim's Rail-to-Rail configuration with common emitters (b).

The bipolar transistors' emitter-collector saturation voltage in these Rail-to-Rail outputs depends on current through the transistors, so the output swing is dependent on the amplifier's output load. Output stages in the MAX4240 family, for instance, swing to within 40mV of the rails (typically) while driving loads as high as 10k Ω . Even with a 100k Ω load, the MAX4240 (configured as a voltage follower operating on a 2V single supply) offers typical output swings between V_{EE} + 6mV and V_{CC} - 8mV.

Related Parts

MAX4041	Single/Dual/Quad, Low-Cost, SOT23, Micropower Rail-to-Rail I/O Op Amps	Free Samples
MAX4042	Single/Dual/Quad, Low-Cost, SOT23, Micropower Rail-to-Rail I/O Op Amps	Free Samples
MAX4162	SOT23, Micropower, Single-Supply, Rail-to-Rail I/O Op Amps	Free Samples
MAX4163	SOT23, Micropower, Single-Supply, Rail-to-Rail I/O Op Amps	Free Samples
MAX4240	Single/Dual/Quad, +1.8V/10 μ A, SOT23, Beyond-the-Rails Op Amps	Free Samples
MAX4242	Single/Dual/Quad, +1.8V/10 μ A, SOT23, Beyond-the-Rails Op Amps	Free Samples
MAX4291	Ultra-Small, +1.8V, μ Power, Rail-to-Rail I/O Op Amps	Free Samples
MAX4292	Ultra-Small, +1.8V, μ Power, Rail-to-Rail I/O Op Amps	Free Samples
MAX492	Single/Dual/Quad, Micropower, Single-Supply, Rail-to-Rail Op Amps	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 741: <http://www.maximintegrated.com/an741>

TUTORIAL 741, AN741, AN 741, APP741, Appnote741, Appnote 741

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>