



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Digital Potentiometers](#) > APP 843

Keywords: industrial digital pots, industrial digital potentiometer, 10V pot, 10V potentiometer, MAX5160, potentiometers

APPLICATION NOTE 843

Industrial 0V to +10V Digital Potentiometer

By: **Phill Leyva**

Nov 02, 2001

Abstract: AC and DC motors in modern industrial systems are often controlled via programmable logic controllers (PLCs) where an industrial mechanical potentiometer controls the motor speed. The wiper of these potentiometers can become worn over a period of time. This article discusses a simple circuit using few solid-state surface mount devices. It uses a digital potentiometer to achieve the same performance, eliminates problems with wiper contacts wearing out, and saves money in the long run.

DC and AC motors in modern industrial systems are often controlled by programmable logic controllers (PLCs) located in a control room safely away from the process. If an operator must set the motor speed manually while observing the process, the component of choice is usually an industrial-grade potentiometer, whose wiper produces a 0V to 10V signal that feeds back to a motor controller in the control room. Such potentiometers are expensive and prone to wear. With wear they can open the control loop, allowing the motor speed to ramp up and out of control.

With a few components, a reliable, low-cost, all-surface-mount, solid-state digital potentiometer can be implemented for industrial applications (**Figure 1**). The result is a direct drop-in replacement for the wear-prone mechanical potentiometer, and it occupies the same space within an electrical enclosure. It takes power from the +10V formerly supplied to the mechanical pot from the motor controller. The solid-state pot provides a similar 0V to 10V output, and delivers as much as 15mA to the controller.

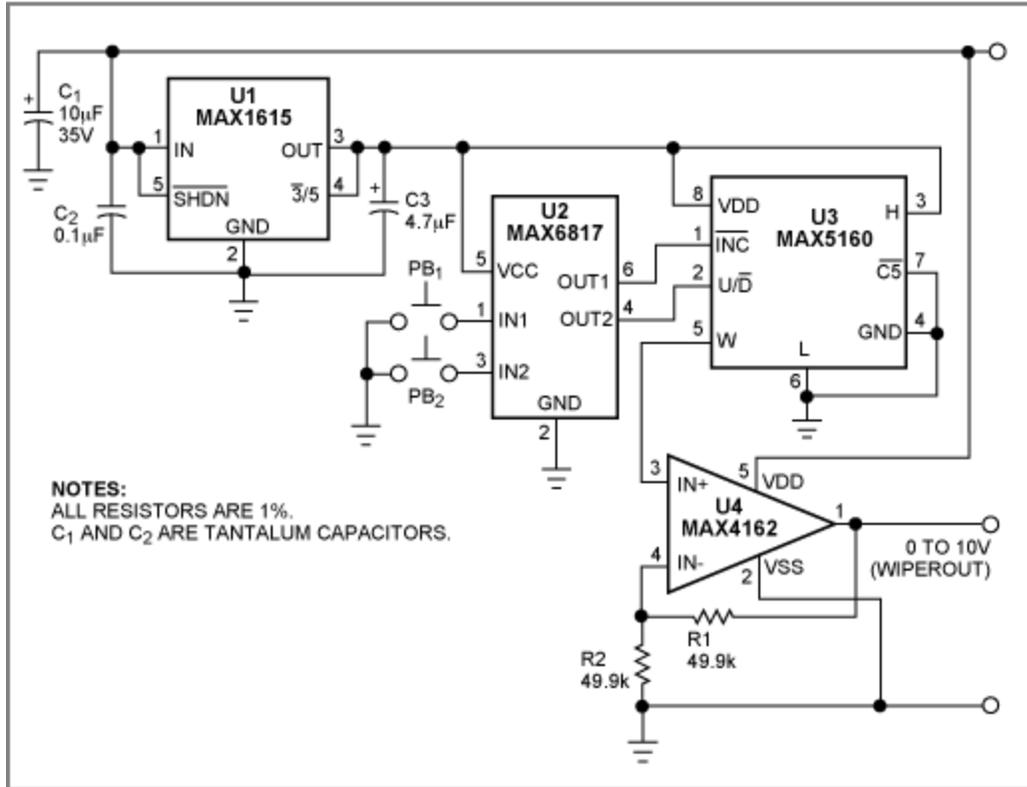


Figure 1. This solid-state industrial potentiometer simulates an equivalent mechanical potentiometer, and fits in the same space.

The key to this circuit is a low-power digital potentiometer IC, 100kΩ version (U3). Configured as a voltage divider, this IC provides an output of 32 discrete voltage steps between its minimum and maximum settings (0V and 5V). A low-power linear regulator (U1) provides a +5V supply rail for U2, U3, and a resistor ladder internal to U3 (whose maximum rating is +5V).

PB1 and PB2 constitute a double-pushbutton industrial switch. Each high-to-low transition produced by PB1 increments the digital potentiometer's "wiper" by one step (depressing PB2 while toggling PB1 decrements the wiper by one step). U2 is a switch debouncer that provides (in addition to the debouncing) a 40ms fixed delay between its outputs and the switch action.

To provide 0V to +10V outputs as required by the motor controller, a single-supply, rail-to-rail op amp (U4) amplifies the U3 output by a factor of two. The input common-mode range for this op amp, (250mV beyond either supply rail), allows it to generate 0V to +10V outputs like a mechanical potentiometer. The 1% resistors R1 and R2 set the op amp gain to 2V/V.

The circuit's low quiescent current ranges from 86µA for a 0V output to 186µA at +10V. To lower this quiescent current, choose the 200kΩ version of U3. Because the op amp is stable for any capacitive load, it easily drives long, shielded, multi-conductor cable runs back to the control room. Another benefit of the all-surface-mount solid-state construction is important for Class 2 enclosures: its lower power dissipation produces less heat within the electrical enclosure.

A similar version of this article appeared in the September 20, 2001 issue of *EDN* magazine.

Related Parts

| | | |
|-------------------------|--|------------------------------|
| MAX1615 | High-Voltage, Low-Power Linear Regulators for Notebook Computers | Free Samples |
| MAX4162 | SOT23, Micropower, Single-Supply, Rail-to-Rail I/O Op Amps | Free Samples |
| MAX5160 | Low-Power Digital Potentiometers | Free Samples |
| MAX6817 | ±15kV ESD-Protected, Single/Dual/Octal, CMOS Switch Debouncers | Free Samples |

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 843: <http://www.maximintegrated.com/an843>

APPLICATION NOTE 843, AN843, AN 843, APP843, Appnote843, Appnote 843

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>