

Keywords: step down regulator, PWM, PFM, negative step-down regulator, DC-DC, dc-dc

APPLICATION NOTE 945

Step-Up Controller Forms Negative Step-Down Regulator

Jan 31, 2002

Abstract: This application note demonstrates how to form a negative step-down switching regulator from a step-up switching controller, using the MAX1771, a high-efficiency, step-up DC-DC controller operating in pulse-frequency modulation (PFM) mode.

A similar version of this article appeared in the September 6, 1999 issue of *EE Times* magazine.

Positive step-down switching regulators are common, but the complementary negative step-down function (converting a negative voltage to a smaller negative voltage) is rare by comparison.

Figure 1 shows a negative step-down switching regulator that delivers 1A at -7.5V from -15V, with efficiency better than 90%. The IC is a step-up switching controller referenced to the negative rail.

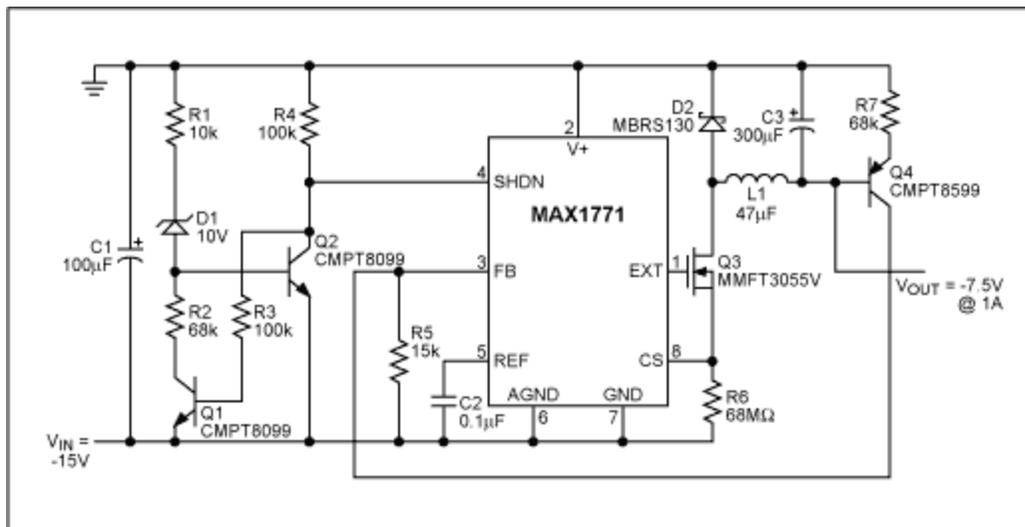


Figure 1. This negative step-down circuit regulates -15V down to -7.5V.

When the power switch (Q3) turns on, the current in L1 increases as long as V_{OUT} is less negative than V_{IN} . When this inductor current reaches the limit set by R6, Q3 turns off. Q3's drain flies high and is clamped to the positive supply rail (ground) by the catch diode (D2). Inductor current then decreases until Q3 turns on again. The output capacitor (C3) integrates inductor current to produce the output

voltage.

Output voltage is referenced to the positive supply rail, and Q4 reflects the error signal from the positive rail to the negative rail. When the error signal falls below the feedback threshold, the power switch turns on and initiates another switching cycle.

D1, Q1, Q2, and R1-R4 form a startup circuit that holds IC1 in shutdown until V_{IN} reaches approximately -11V. This action ensures that Q4 has sufficient voltage compliance to regulate the feedback loop. The minimum input voltage necessary to maintain a regulated output voltage is $V_{OUT} + (-V_{FB})$, where V_{FB} is the feedback threshold voltage (1.5V in this case). Efficiency varies with load current as shown in **Figure 2**.

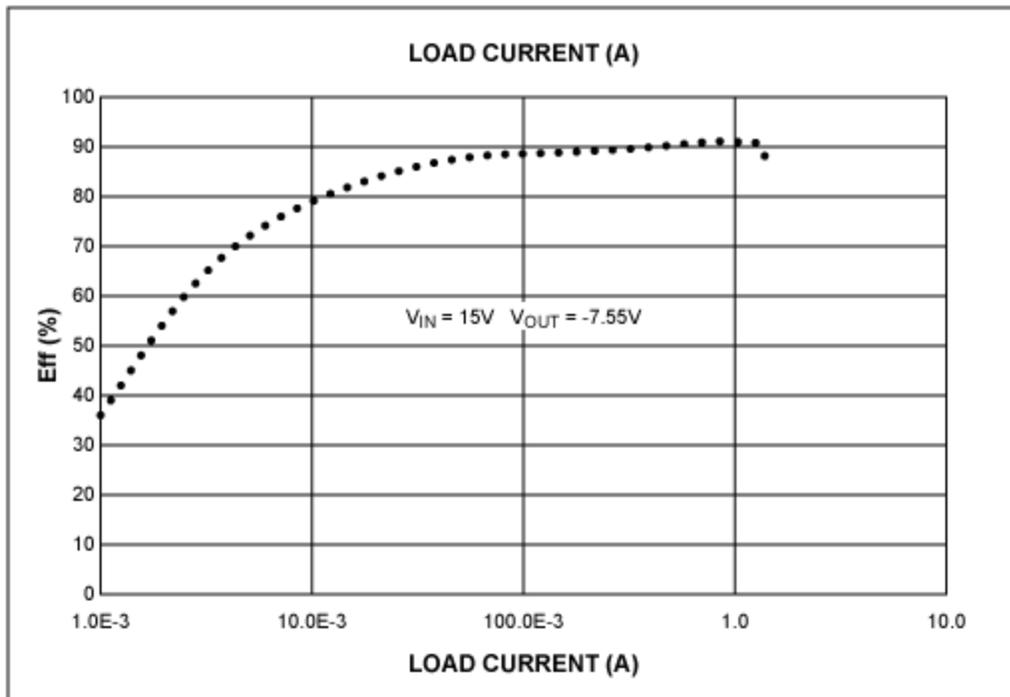


Figure 2. Conversion efficiency for the Figure 1 circuit rises with load current.

The MAX1771 controller IC used in this circuit operates in the pulse-frequency modulation (PFM) mode. The MAX668 controller IC, which operates in the pulse-width modulation (PWM) mode, could be used in a similar circuit to step-down a negative voltage. PWM controllers offer the advantage of fixed-frequency operation. The MAX668 controller offers the further advantage of coming in a smaller package than the MAX1771 PFM controller.

Related Parts

MAX1771	12V or Adjustable, High-Efficiency, Low I_Q , Step-Up DC-DC Controller	Free Samples
MAX668	1.8V to 28V Input, PWM Step-Up Controllers in μ MAX	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>
For Samples: <http://www.maximintegrated.com/samples>
Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 945: <http://www.maximintegrated.com/an945>
APPLICATION NOTE 945, AN945, AN 945, APP945, Appnote945, Appnote 945
Copyright © by Maxim Integrated Products
Additional Legal Notices: <http://www.maximintegrated.com/legal>