

Keywords: avalanche photodiode detector, APD, APD bias generator, DC-DC controller, boost converter

APPLICATION NOTE 990

APD Bias Circuit Has Adjustable Output

May 22, 1997

Abstract: This design note discusses the role of an avalanche photodiode detector (APD) and the importance of APD bias generation. It shows an APD bias generator that produces a regulated, computer-adjusted output in the 30V to 70V range. The MAX1771 step-up DC-DC controller is featured.

A similar idea appeared in the May 22, 1997 issue of EDN.

The avalanche photodiode detector (APD) is used as a receiver in optical communications, as is the pin diode. The APD is more sensitive, but it must be biased properly to produce the appropriate electron flow for a given flux of photons. In **Figure 1**, an external digital-to-analog converter enables dynamic, computer-controlled adjustment of an APD bias generator.

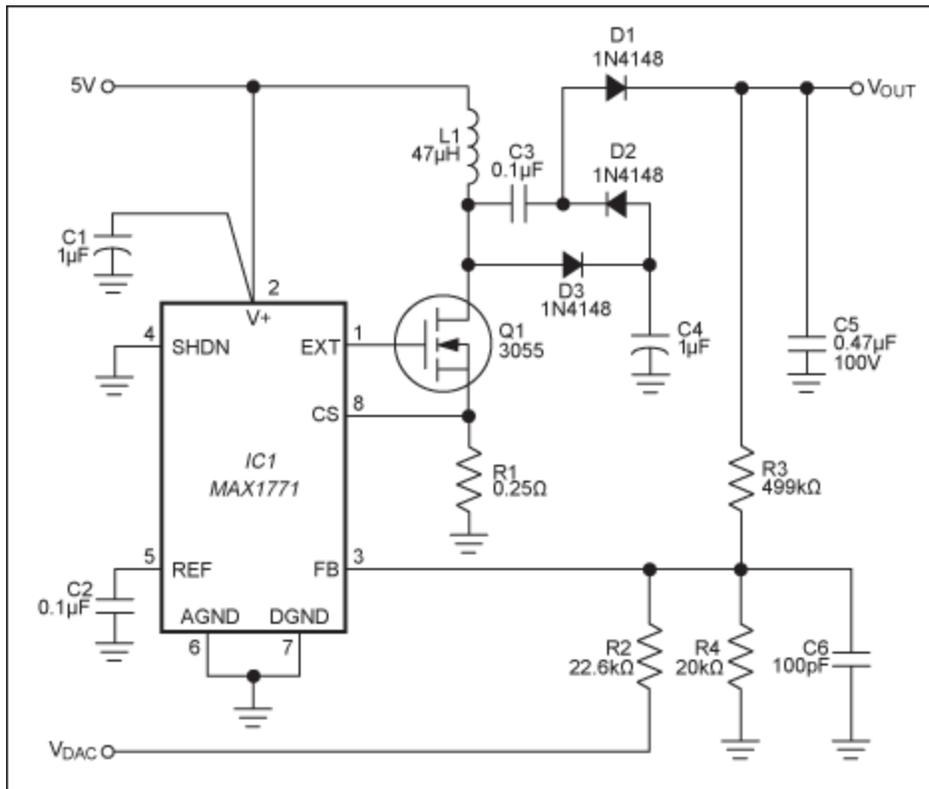


Figure 1. This APD-bias generator produces a regulated, computer-adjusted output in the 30V to 70V range.

To generate the bias voltage V_{OUT} , a boost converter (IC1, L1, and Q1) drives a diode-capacitor charge pump (D3/C4, D2/C3, and D1/C5). IC1 regulates V_{OUT} with respect to a set point established by the external control voltage V_{DAC} : As V_{DAC} ranges from 2V to zero, V_{OUT} varies from 28V to about 71V (Figure 2).

At 70V with a 0.5mA output current, the limitation on ripple is typically 0.5V (max) (0.7%). The circuit shown produces less than 0.3% ripple at 1mA, and its maximum output current is about 3mA. The output capacitor (C5) should be a low-ESR type.

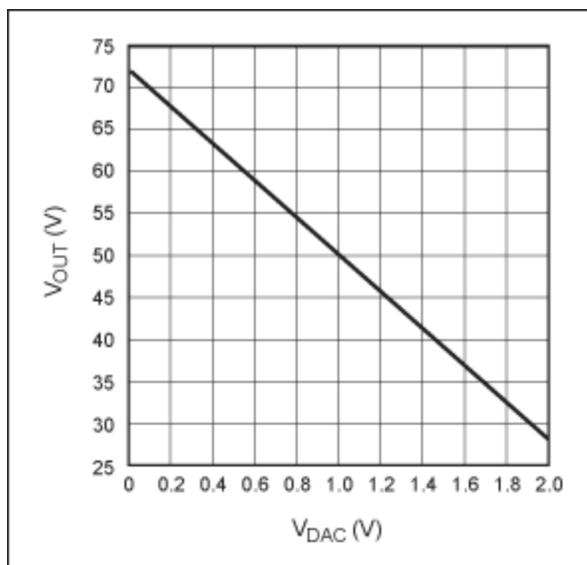


Figure 2. The DC-output level in Figure 1 is a linear function of the control-voltage V_{DAC} .

Related Parts

MAX1771

12V or Adjustable, High-Efficiency, Low I_Q , Step-Up DC-DC Controller

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 990: <http://www.maximintegrated.com/an990>

APPLICATION NOTE 990, AN990, AN 990, APP990, Appnote990, Appnote 990

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>